


Combinational Circuit Design

Chapter 4

Combinational Circuits

★ Output is function of input only

i.e. no feedback

 


When **input** changes, **output** may change (after a delay)

Combinational Circuits


★ Analysis

 - Given a circuit, find out its *function*
- Function may be expressed as:
 - ◆ Boolean function
 - ◆ Truth table




★ Design

 - Given a desired function, determine its *circuit*
- Function may be expressed as:
 - ◆ Boolean function
 - ◆ Truth table



Analysis Procedure

★ Boolean Expression Approach

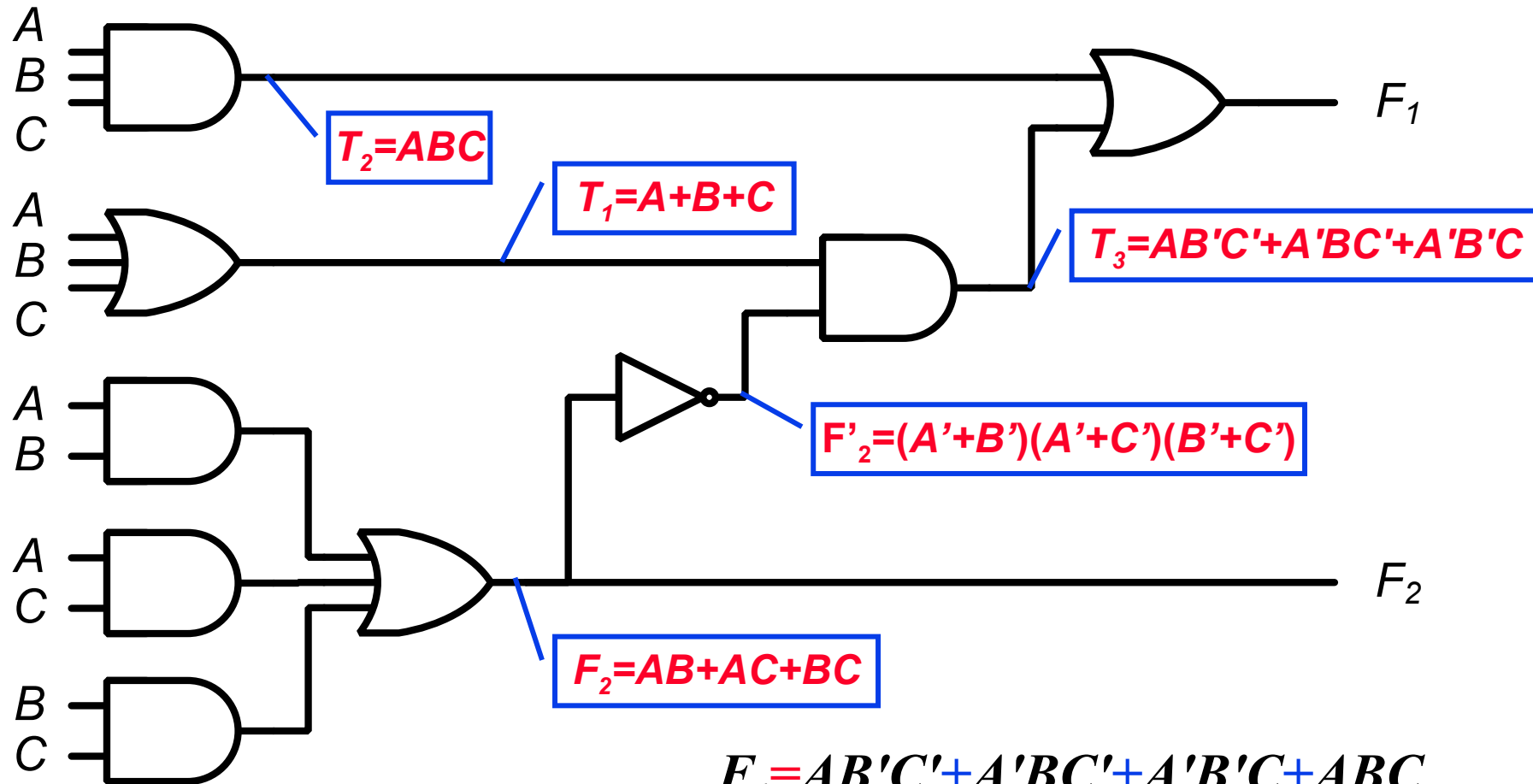


$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Analysis Procedure


★ Truth Table Approach

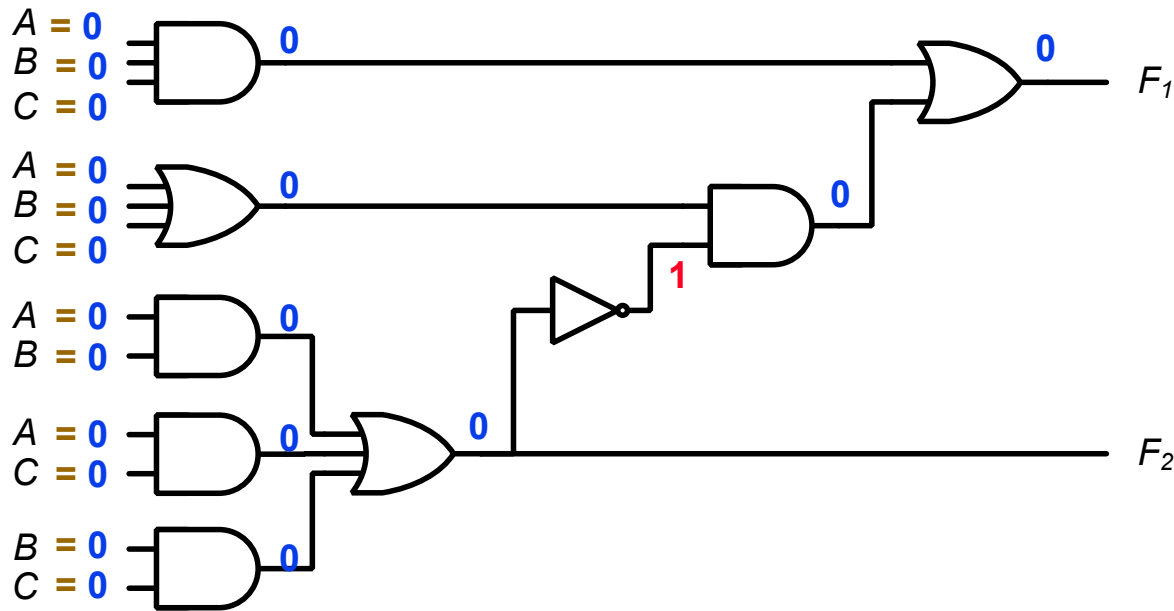

A	B	C	F_1	F_2
0	0	0	0	0

Analysis Procedure


★ Truth Table Approach

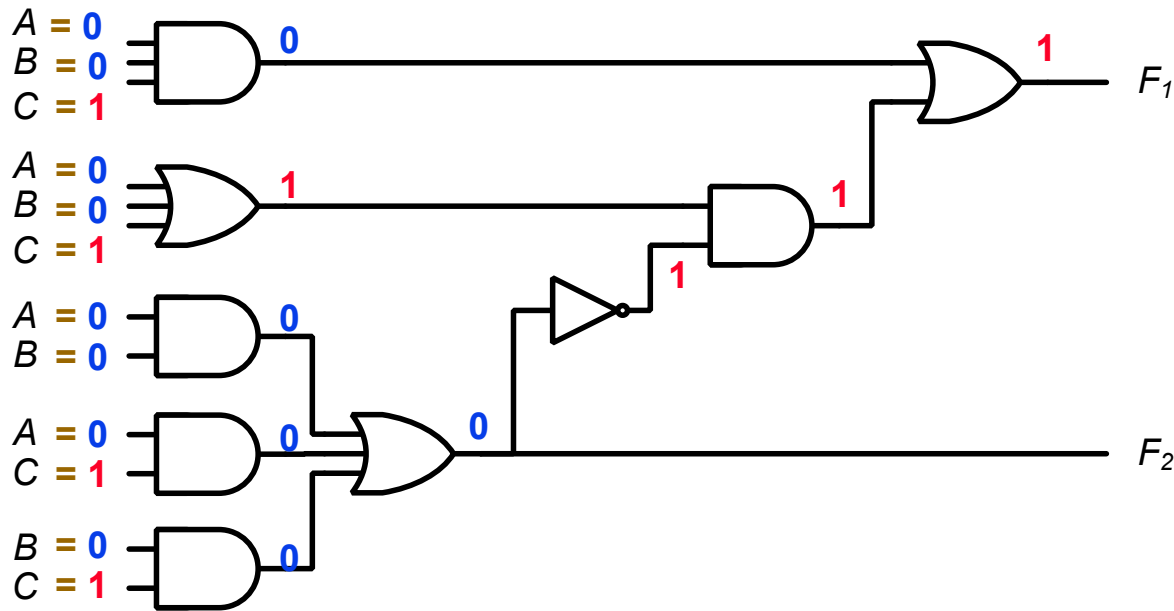

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0

Analysis Procedure


★ Truth Table Approach

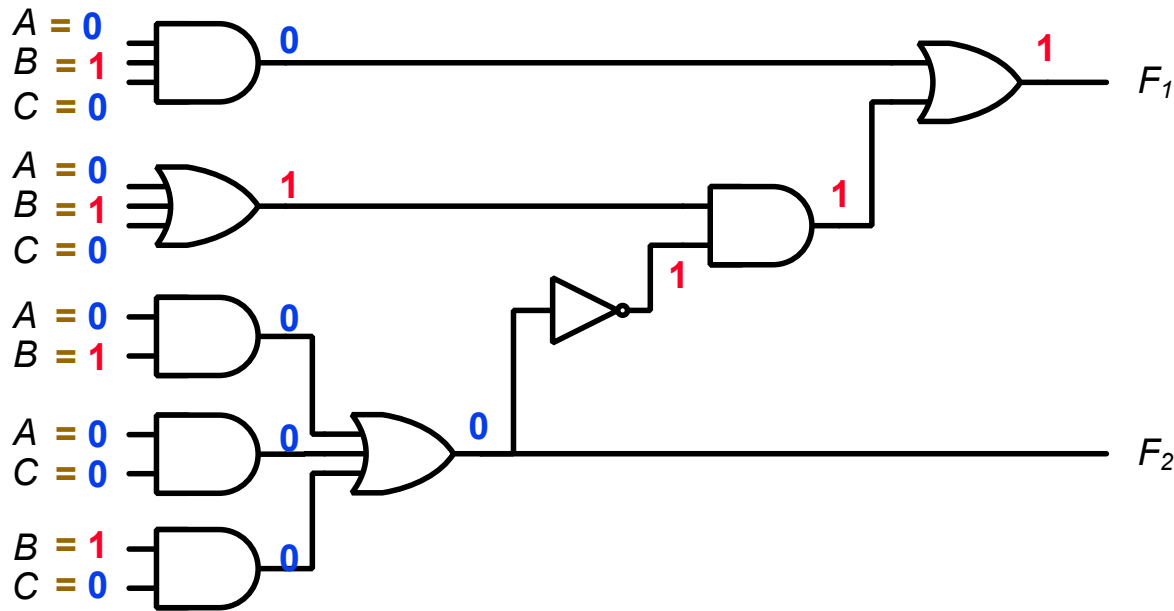

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0

Analysis Procedure


★ Truth Table Approach

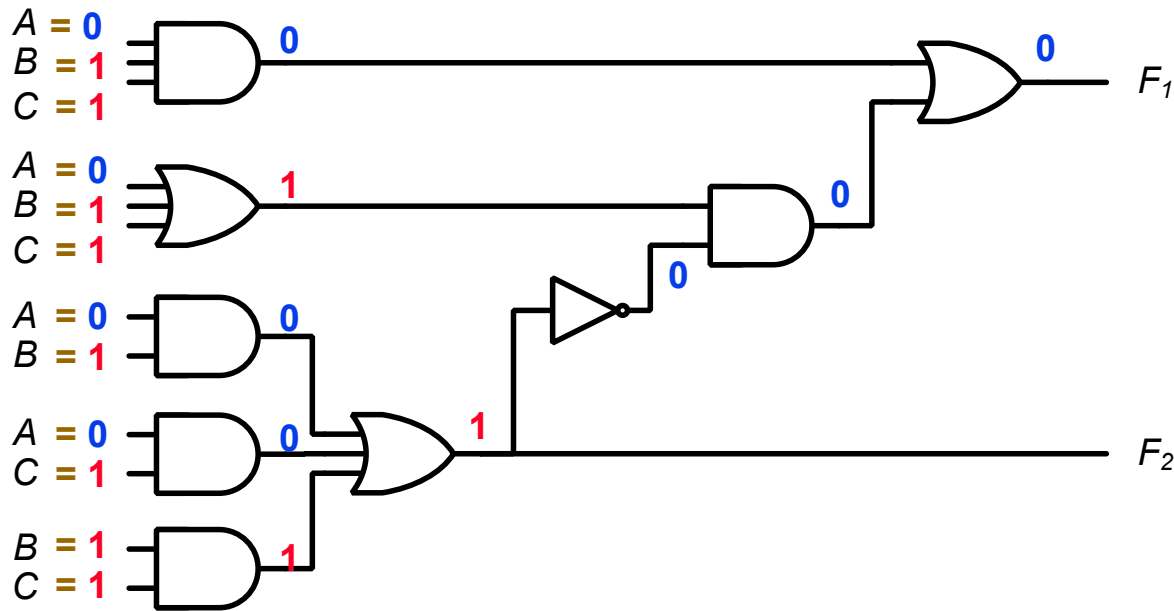

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1

Analysis Procedure


★ Truth Table Approach

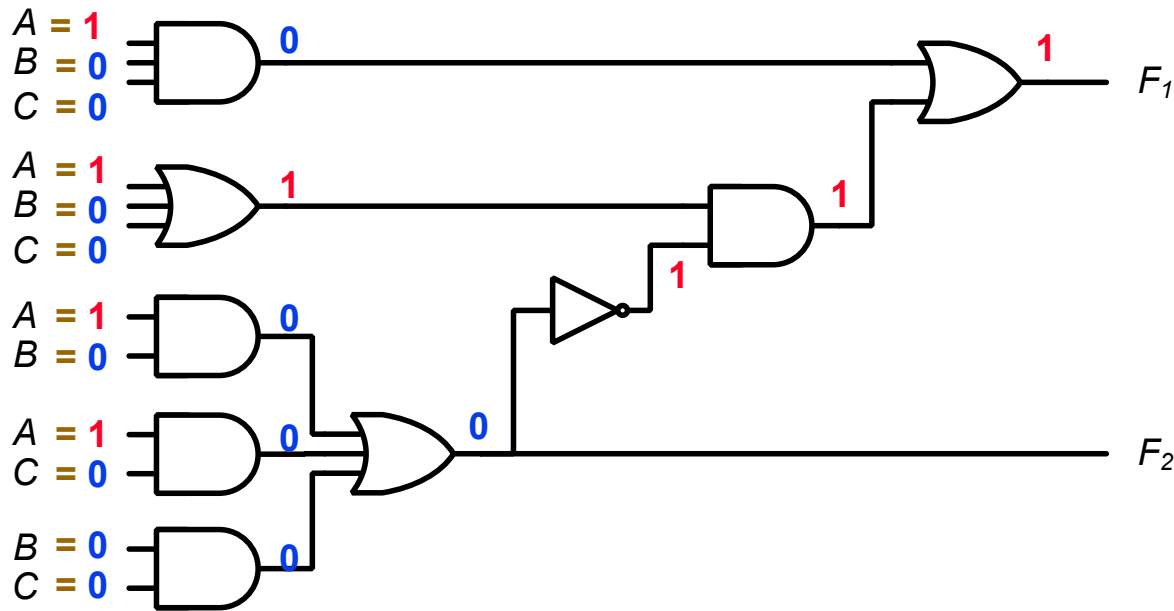

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

Analysis Procedure


★ Truth Table Approach

 

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1

Analysis Procedure


★ Truth Table Approach

 

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1

Analysis Procedure

★ Truth Table Approach

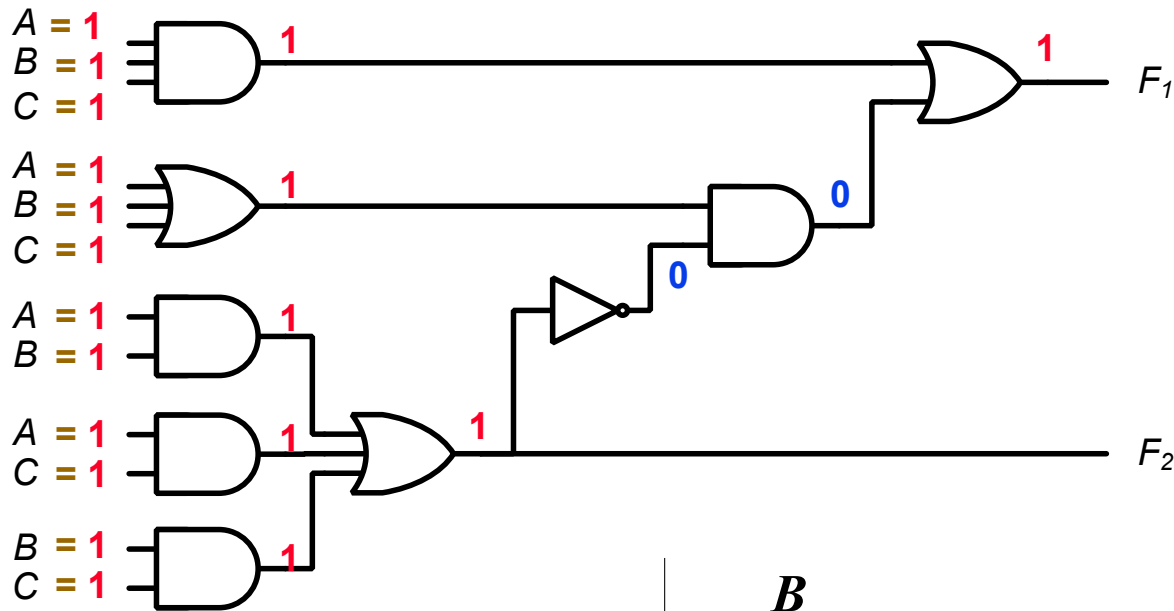

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

			B	
			0	1
			0	1
			1	0
			1	0
A				
			C	

			B	
			0	0
			1	1
			1	1
			0	1
A				
			C	

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$


Design Procedure

★ Given a problem statement:

- Determine the number of *inputs* and *outputs*
- Derive the truth table
- Simplify the Boolean expression for each output
- Produce the required circuit

 Example:


Design a circuit to convert a “BCD” code to “Excess 3” code




Design Procedure

★ BCD-to-Excess 3 Converter


<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

 


$$w = A + BC + BD$$

 

$$x = B'C + B'D + BC'D'$$

 

$$y = C'D' + CD$$

 


$$z = D'$$

Design Procedure

★ BCD-to-Excess 3 Converter

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

 

$$w = A + B(C+D)$$




$$x = B'(C+D) + B(C+D)'$$

$$y = (C+D)' + CD$$

$$z = D'$$

Seven-Segment Decoder

<i>w x y z</i>	<i>a b c d e f g</i>
0 0 0 0	1 1 1 1 1 1 0
0 0 0 1	0 1 1 0 0 0 0
0 0 1 0	1 1 0 1 1 0 1
0 0 1 1	1 1 1 1 0 0 1
0 1 0 0	0 1 1 0 0 1 1
0 1 0 1	1 0 1 1 0 1 1
0 1 1 0	1 0 1 1 1 1 1
0 1 1 1	1 1 1 0 0 0 0
1 0 0 0	1 1 1 1 1 1 1
1 0 0 1	1 1 1 1 0 1 1
1 0 1 0	x x x x x x x
1 0 1 1	x x x x x x x
1 1 0 0	x x x x x x x
1 1 0 1	x x x x x x x
1 1 1 0	x x x x x x x
1 1 1 1	x x x x x x x

   

$$a = w + y + xz + x'z'$$

$$b = \dots$$

$$c = \dots$$


$$d = \dots$$

Binary Adder


★ Half Adder

- Adds **1-bit** plus **1-bit**
- Produces **Sum** and **Carry**

x y	C S
0 0	0 0
0 1	0 1
1 0	0 1
1 1	1 0

 

 
$$\begin{array}{r} x \\ + y \\ \hline C \quad S \end{array}$$



Binary Adder

★ Full Adder

 - Adds **1-bit** plus **1-bit** plus **1-bit**
- Produces **Sum** and **Carry**



$$\begin{array}{r}
 x \\
 + y \\
 + z \\
 \hline
 C \quad S
 \end{array}$$

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

			y
	0	1	0
x	1	0	1

$$S = xy'z' + x'y'z + x'yz + xyz = x \oplus y \oplus z$$

			y
	0	0	1
x	0	1	1



$$C = xy + xz + yz$$

Binary Adder

★ Full Adder



$$S = xy'z' + x'yz' + x'y'z + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

 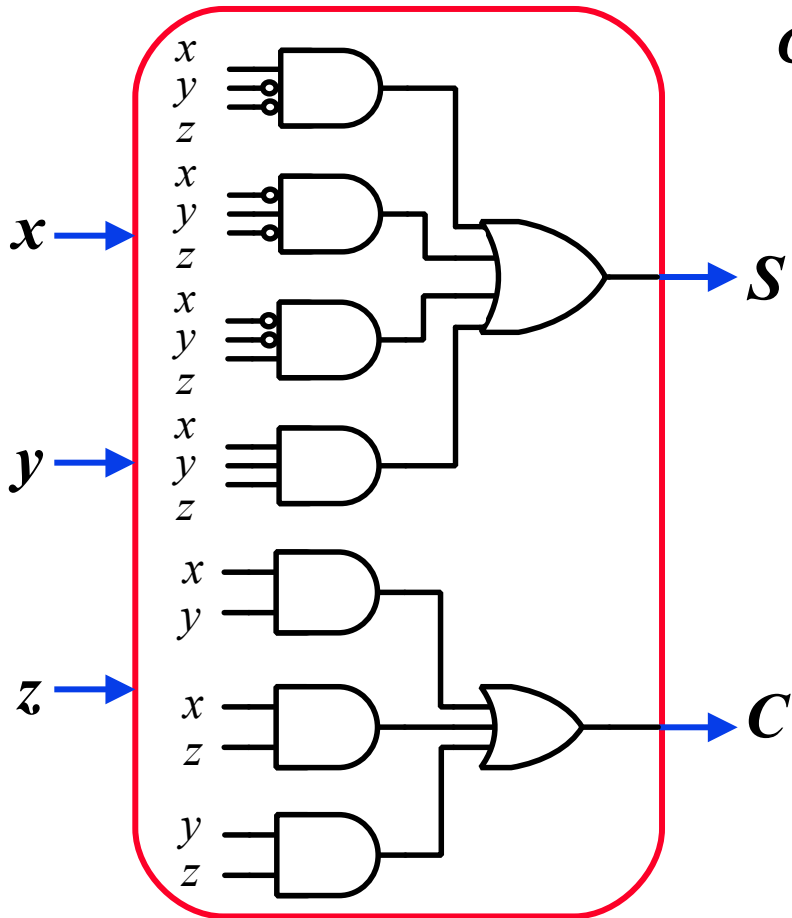


Binary Adder

★ Full Adder

  


Binary Adder

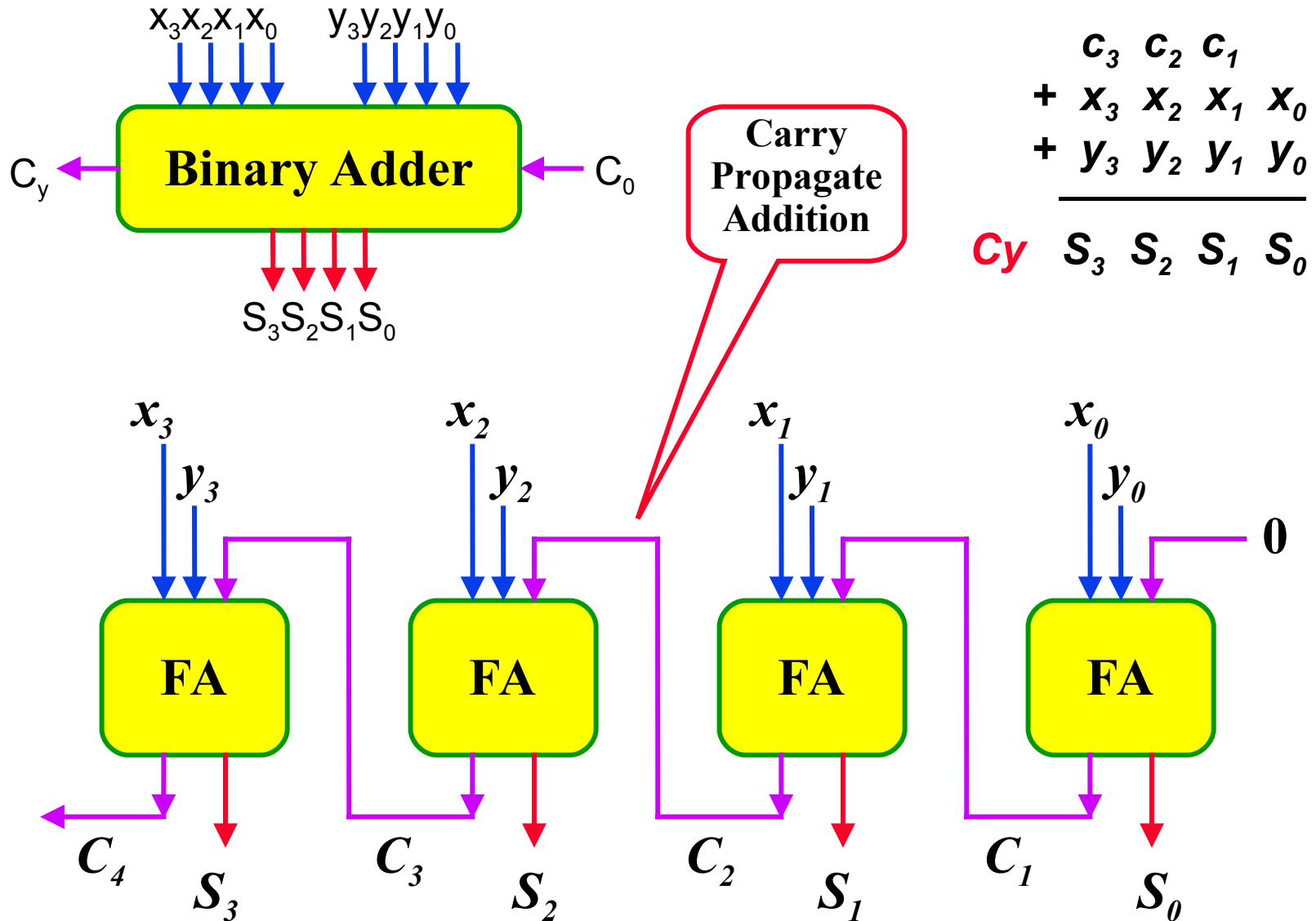

Binary Adder

★ Carry Propagate Adder

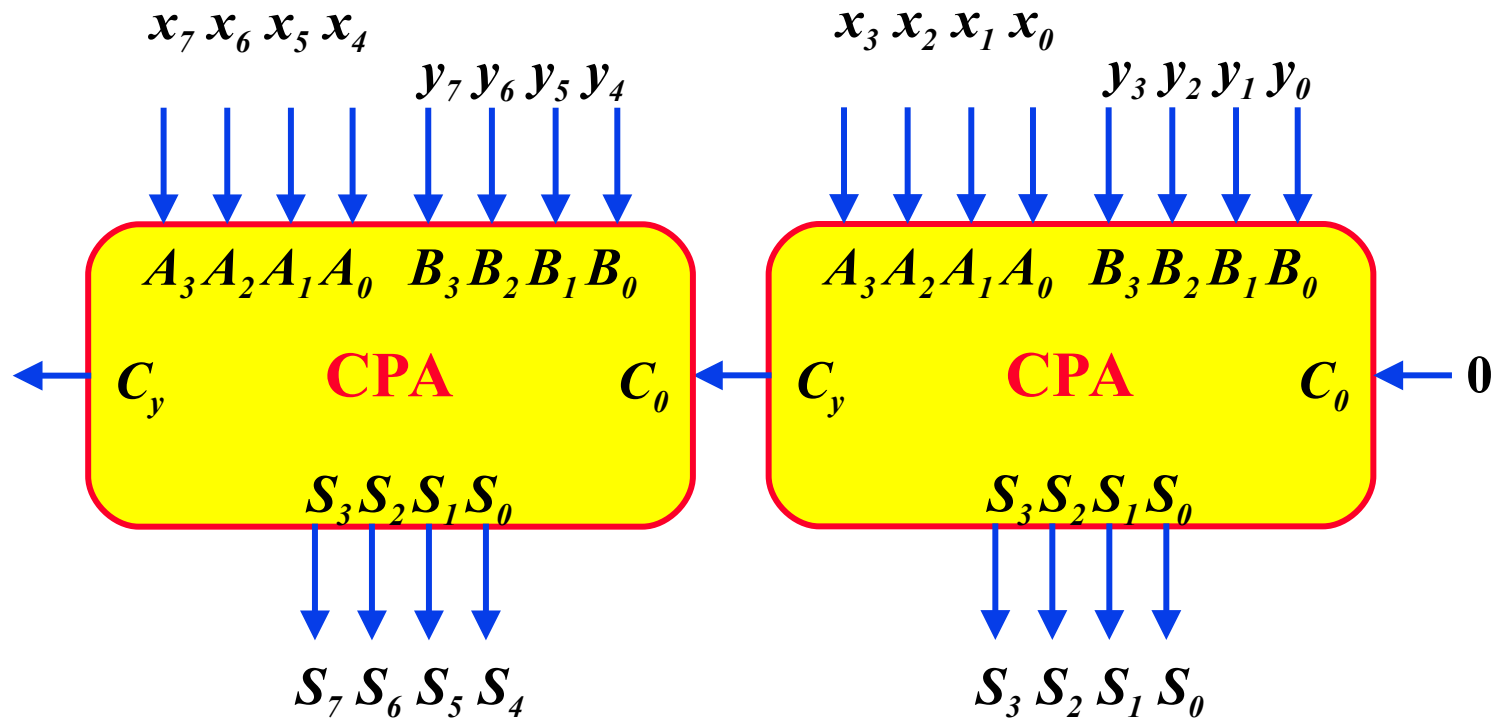

★ Carry propagation

- When the correct outputs are available
- The critical path counts (the worst case)
- $(A_1, B_1, C_1) \rightarrow C_2 \rightarrow C_3 \rightarrow C_4 \rightarrow (C_5, S_4)$
- When 4-bits full-adder \rightarrow 8 gate levels (n -bits: $2n$ gate levels)


 


Figure 4.10 Full Adder with P and G Shown

Parallel Adders

★ Reduce the carry propagation delay

- Employ faster gates
- Look-ahead carry (more complex mechanism, yet faster)
- Carry propagate: $P_i = A_i \oplus B_i$
- Carry generate: $G_i = A_i B_i$
- Sum: $S_i = P_i \oplus C_i$
- Carry: $C_{i+1} = G_i + P_i C_i$
- $C_0 = \text{Input carry}$
- $C_1 = G_0 + P_0 C_0$
- $C_2 = G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$
- $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

 

Carry Look-ahead Adder (1/2)

★ Logic diagram

 


Fig. 4.11 Logic Diagram of Carry Look-ahead Generator

Carry Look-ahead Adder (2/2)

★ 4-bit carry-look ahead adder

- Propagation delay of C_3 , C_2 and C_1 are equal.

 


Fig. 4.12 4-Bit Adder with Carry Look-ahead

BCD Adder

★ 4-bits plus 4-bits

★ Operands and Result: 0 to 9

$$\begin{array}{r} + x_3 \ x_2 \ x_1 \ x_0 \\ + y_3 \ y_2 \ y_1 \ y_0 \\ \hline \end{array}$$

$$\text{Cy} \quad s_3 \ s_2 \ s_1 \ s_0$$

$X+Y$	$x_3 \ x_2 \ x_1 \ x_0$	$y_3 \ y_2 \ y_1 \ y_0$	Sum	Cy	$s_3 \ s_2 \ s_1 \ s_0$
0 + 0	0 0 0 0	0 0 0 0	= 0	0	0 0 0 0
0 + 1	0 0 0 0	0 0 0 1	= 1	0	0 0 0 1
0 + 2	0 0 0 0	0 0 1 0	= 2	0	0 0 1 0
0 + 9	0 0 0 0	1 0 0 1	= 9	0	1 0 0 1
1 + 0	0 0 0 1	0 0 0 0	= 1	0	0 0 0 1
1 + 1	0 0 0 1	0 0 0 1	= 2	0	0 0 1 0
1 + 8	0 0 0 1	1 0 0 0	= 9	0	1 0 0 1
1 + 9	0 0 0 1	1 0 0 1	= A	0	1 0 1 0
2 + 0	0 0 1 0	0 0 0 0	= 2	0	0 0 1 0
9 + 9	1 0 0 1	1 0 0 1	= 12	1	0 0 1 0

Invalid Code

Wrong BCD Value

0001 1000

BCD Adder

$X+Y$	$x_3 x_2 x_1 x_0$	$y_3 y_2 y_1 y_0$	Sum	Cy	$S_3 S_2 S_1 S_0$	Required BCD Output	Value
9 + 0	1 0 0 1	0 0 0 0	= 9	0	1 0 0 1	0 0 0 0 1 0 0 1	= 9
9 + 1	1 0 0 1	0 0 0 1	= 10	0	1 0 1 0	0 0 0 1 0 0 0 0	= 16
9 + 2	1 0 0 1	0 0 1 0	= 11	0	1 0 1 1	0 0 0 1 0 0 0 1	= 17
9 + 3	1 0 0 1	0 0 1 1	= 12	0	1 1 0 0	0 0 0 1 0 0 1 0	= 18
9 + 4	1 0 0 1	0 1 0 0	= 13	0	1 1 0 1	0 0 0 1 0 0 1 1	= 19
9 + 5	1 0 0 1	0 1 0 1	= 14	0	1 1 1 0	0 0 0 1 0 1 0 0	= 20
9 + 6	1 0 0 1	0 1 1 0	= 15	0	1 1 1 1	0 0 0 1 0 1 0 1	= 21
9 + 7	1 0 0 1	0 1 1 1	= 16	1	0 0 0 0	0 0 0 1 0 1 1 0	= 22
9 + 8	1 0 0 1	1 0 0 0	= 17	1	0 0 0 1	0 0 0 1 0 1 1 1	= 23
9 + 9	1 0 0 1	1 0 0 1	= 18	1	0 0 1 0	0 0 0 1 1 0 0 0	= 24

✗
✗
✗
✗
✗
✗
✗
✗
✗


+ 6

BCD Adder

★ Correct Binary Adder's Output (+6)


- If the result is between 'A' and 'F'
- If $Cy = 1$

$S_3 S_2 S_1 S_0$	Err
0 0 0 0	0
1 0 0 0	0
1 0 0 1	0
1 0 1 0	1
1 0 1 1	1
1 1 0 0	1
1 1 0 1	1
1 1 1 0	1
1 1 1 1	1

 

$$Err = S_3 S_2 + S_3 S_1$$


BCD Adder

 

Binary Subtractor

★ Use 2's complement with binary adder


- $x - y = x + (-y) = x + y' + 1$

 

Binary Adder/Subtractor


★ M : Control Signal (Mode)

 - $M=0 \rightarrow F = x + y$
- $M=1 \rightarrow F = x - y$




Overflow

★ Unsigned Binary Numbers

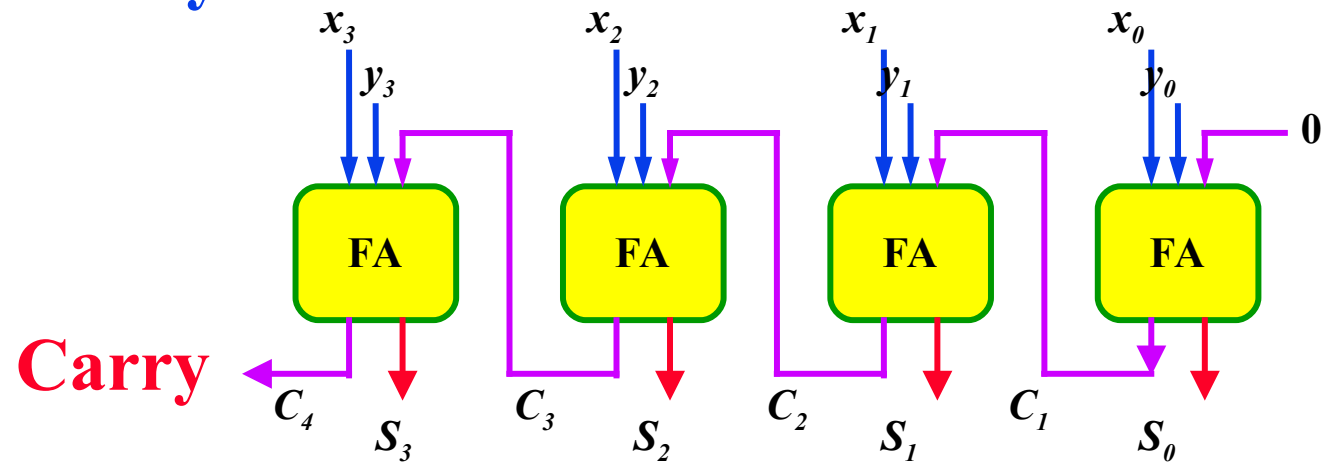

★ 2's Complement Numbers

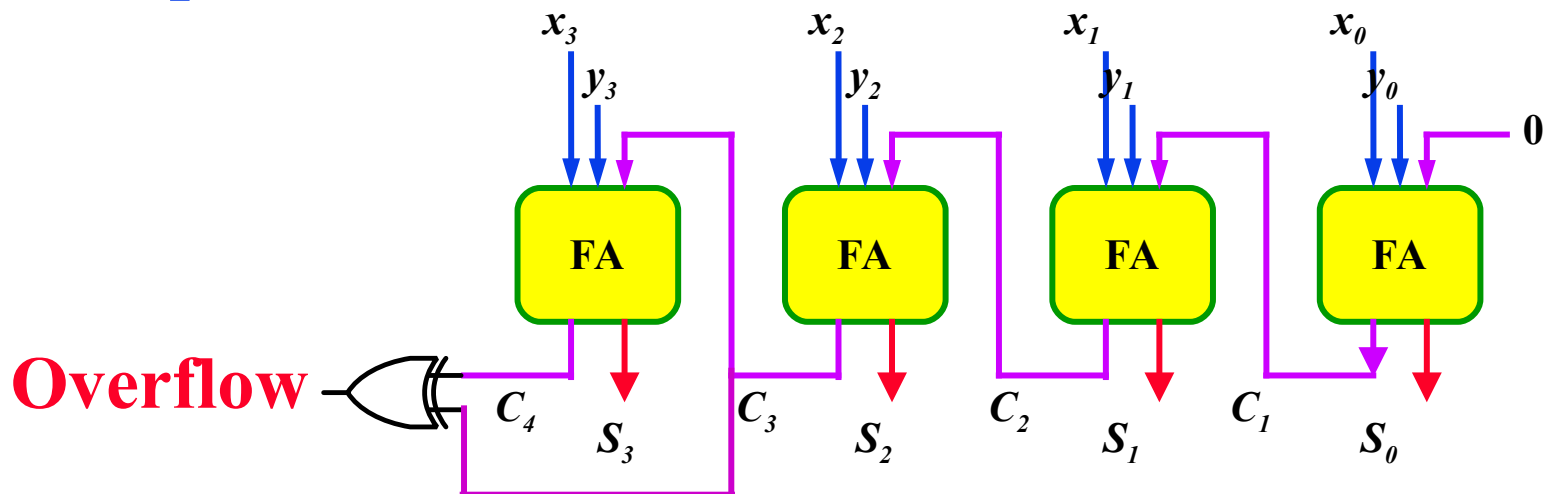

Magnitude Comparator

★ Compare 4-bit number to 4-bit number

- 3 Outputs: $<$, $=$, $>$
- Expandable to more number of bits

$$x_3 = \overline{A_3} \overline{B_3} + A_3 B_3$$

$$x_2 = \overline{A_2} \overline{B_2} + A_2 B_2$$


$$x_1 = \overline{A_1} \overline{B_1} + A_1 B_1$$

$$x_0 = \overline{A_0} \overline{B_0} + A_0 B_0$$


$$(A = B) = x_3 x_2 x_1 x_0$$

$$(A > B) = A_3 \overline{B_3} + x_3 A_2 \overline{B_2} + x_3 x_2 A_1 \overline{B_1} + x_3 x_2 x_1 A_0 \overline{B_0}$$

 
$$(A < B) = \overline{A_3} B_3 + x_3 \overline{A_2} B_2 + x_3 x_2 \overline{A_1} B_1 + x_3 x_2 x_1 \overline{A_0} B_0$$



Magnitude Comparator

 

Magnitude Comparator

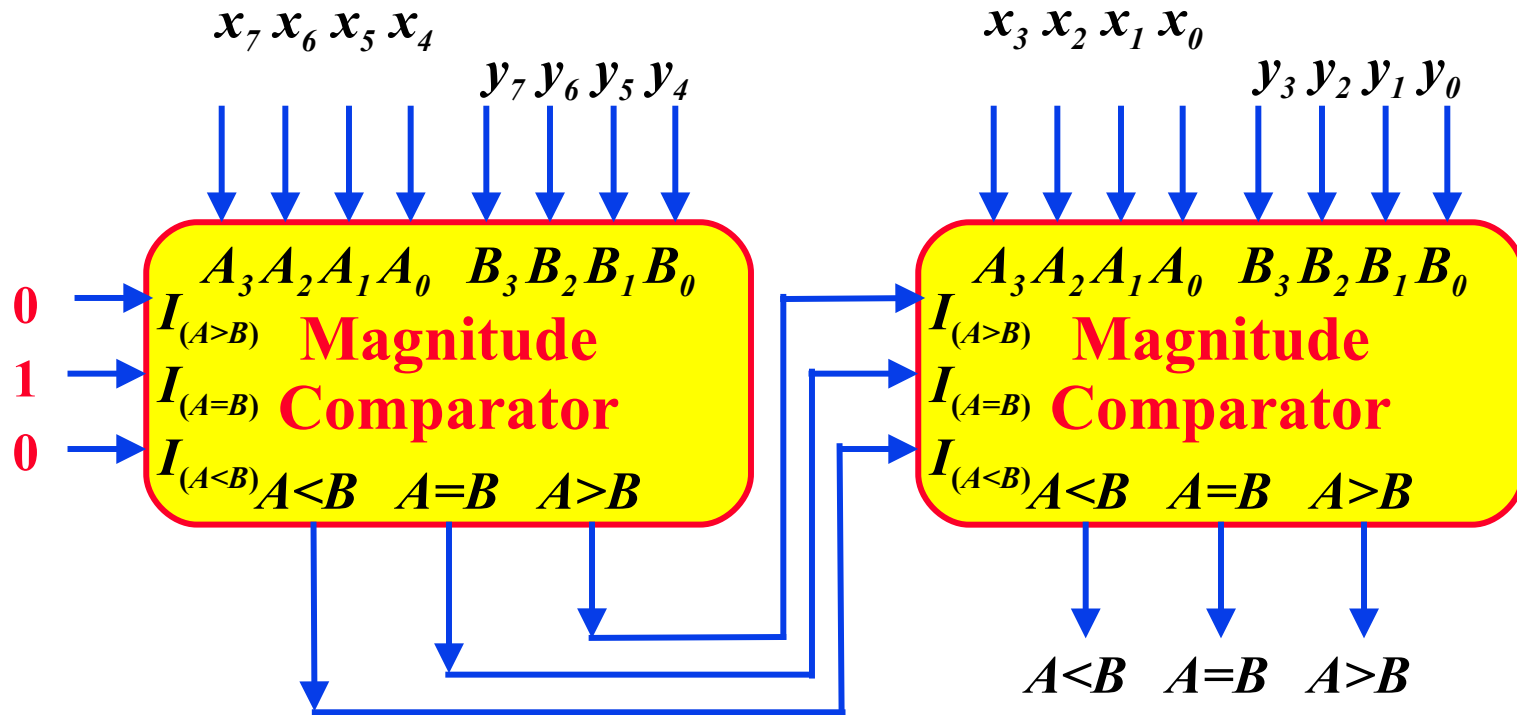


Decoders

★ Extract “*Information*” from the code

★ Binary Decoder


- Example: 2-bit Binary Number

Only *one* lamp will turn on

 


Decoders

★ 2-to-4 Line Decoder

 

I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

$$Y_3 = I_1 I_0$$



$$Y_1 = \bar{I}_1 I_0$$

$$Y_2 = I_1 \bar{I}_0$$

$$Y_0 = \bar{I}_1 \bar{I}_0$$


Decoders

★ 3-to-8 Line Decoder

  


Decoders

★ “Enable” Control

 


E	I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 

Decoders

★ Expansion

$I_2 I_1 I_0$	$Y_7 Y_6 Y_5 Y_4 Y_3 Y_2 Y_1 Y_0$
0 0 0	0 0 0 0 0 0 0 1
0 0 1	0 0 0 0 0 0 1 0
0 1 0	0 0 0 0 0 1 0 0
0 1 1	0 0 0 0 1 0 0 0
1 0 0	0 0 0 1 0 0 0 0
1 0 1	0 0 1 0 0 0 0 0
1 1 0	0 1 0 0 0 0 0 0
1 1 1	1 0 0 0 0 0 0 0



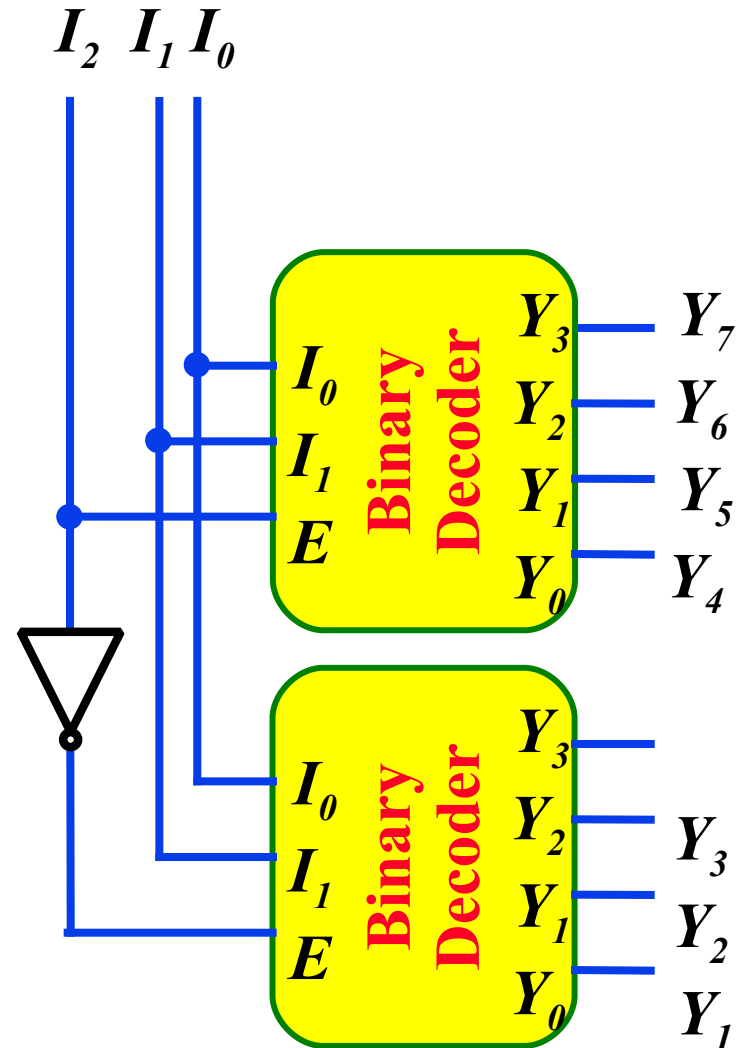


Decoders

★ Active-High / Active-Low

I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	1

   


Implementation Using Decoders

- ★ Each output is a minterm
- ★ All minterms are produced
- ★ Sum the required minterms



Example: **Full Adder**

$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

 

Implementation Using Decoders

  


Encoders

★ Put “*Information*” into code

★ Binary Encoder

- Example: 4-to-2 Binary Encoder

 

Only *one* switch should be activated at a time

x_3	x_2	x_1	y_1	y_0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
1	0	0	1	1

Encoders


★ Octal-to-Binary Encoder (8-to-3)

I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$Y_2 = I_7 + I_6 + I_5 + I_4$$

$$Y_1 = I_7 + I_6 + I_3 + I_2$$


$$Y_0 = I_7 + I_5 + I_3 + I_1$$

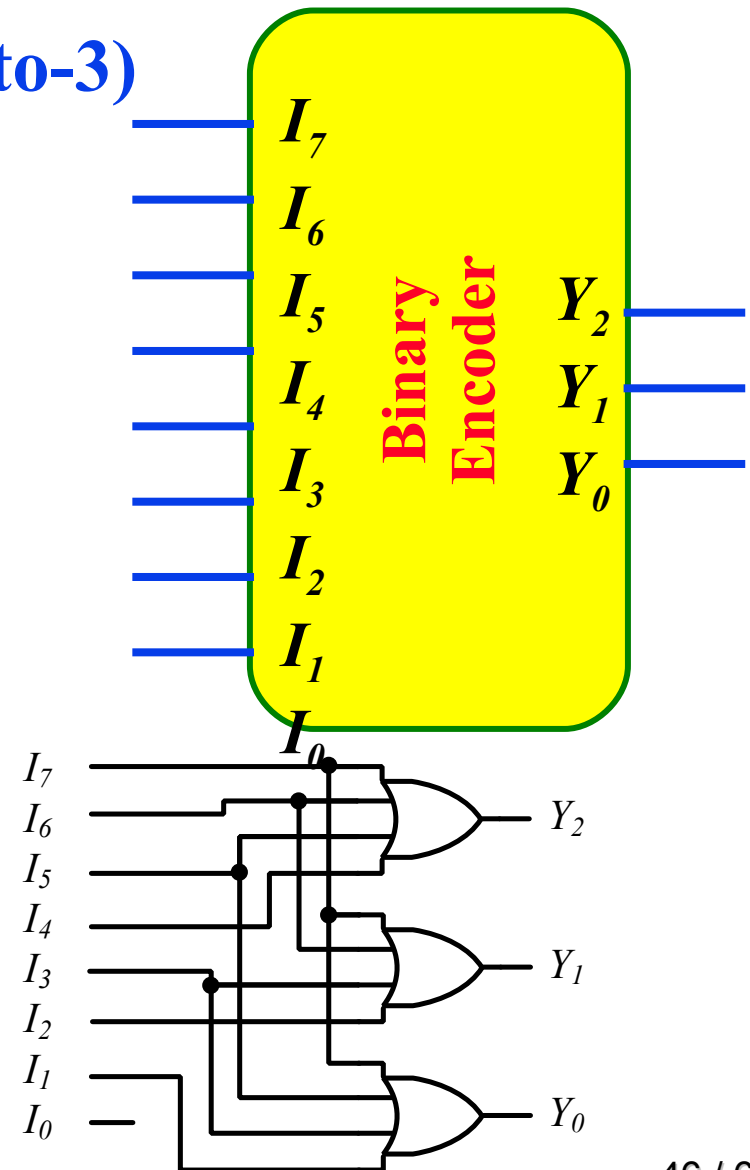

Priority Encoders

★ 4-Input Priority Encoder



I_3	I_2	I_1	I_0	Y_1	Y_0	V
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

 


$$Y_1 = I_3 + I_2$$

$$Y_0 = I_3 + \bar{I}_2 I_1$$


$$V = I_3 + I_2 + I_1 + I_0$$

  


Encoder / Decoder Pairs

 

Multiplexers


 


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


 


Multiplexers

★ 2-to-1 MUX


 
 


★ 4-to-1 MUX

  



Multiplexers

★ Quad 2-to-1 MUX

   

Multiplexers


★ Quad 2-to-1 MUX

 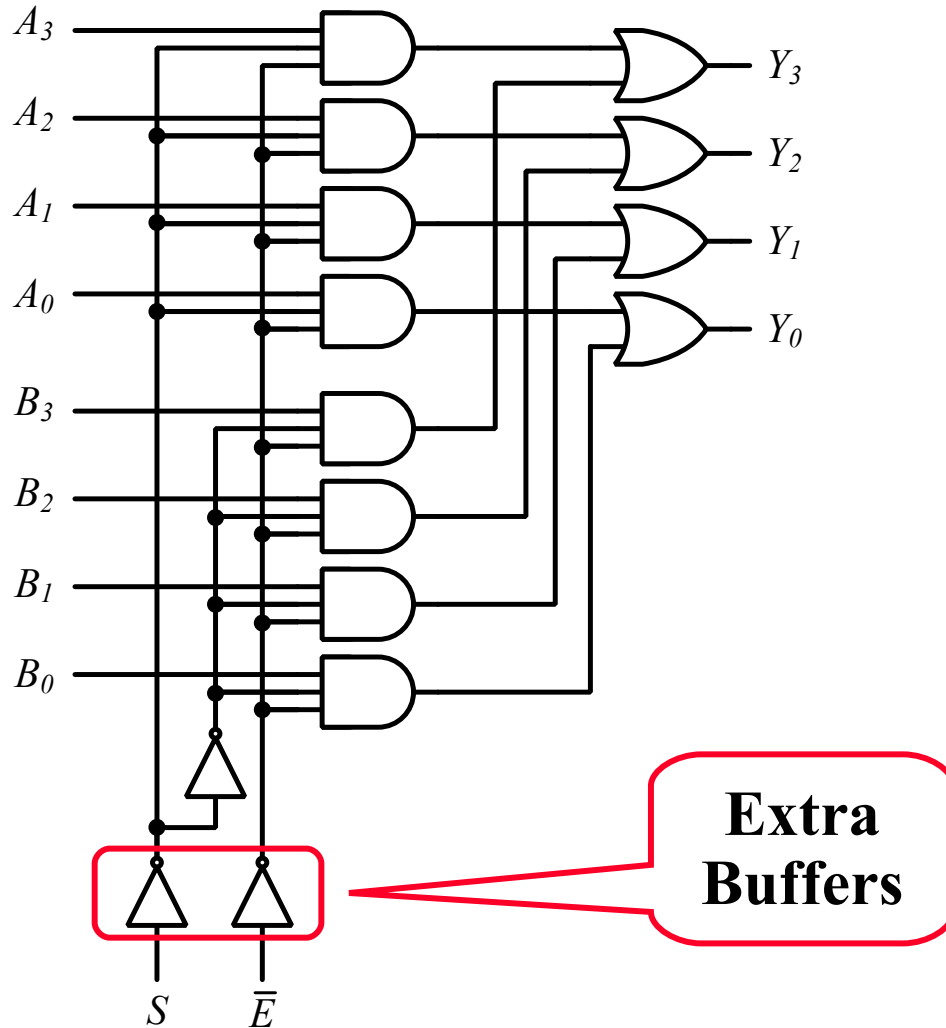

Implementation Using Multiplexers

★ Example

$$F(x, y) = \sum(0, 1, 3)$$

 


Implementation Using Multiplexers

★ Example

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


Implementation Using Multiplexers

★ Example

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 
$\left. \begin{array}{l} F = z \\ F = \bar{z} \\ F = 0 \\ F = 1 \end{array} \right\}$



Implementation Using Multiplexers


★ Example
 
$$F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$$






Multiplexer Expansion

★ 8-to-1 MUX using Dual 4-to-1 MUX

 


DeMultiplexers

  
 


S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0


Multiplexer / DeMultiplexer Pairs

 

DeMultiplexers / Decoders

  

S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

 


E	I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0




Three-State Gates


★ Tri-State Buffer

 


C	A	Y
0	x	Hi-Z
1	0	0
1	1	1

 

★ Tri-State Inverter

 


Three-State Gates

 

<i>C</i>	<i>D</i>	<i>Y</i>
0	0	Hi-Z
0	1	<i>B</i>
1	0	<i>A</i>
1	1	?

Not Allowed

 

Three-State Gates

