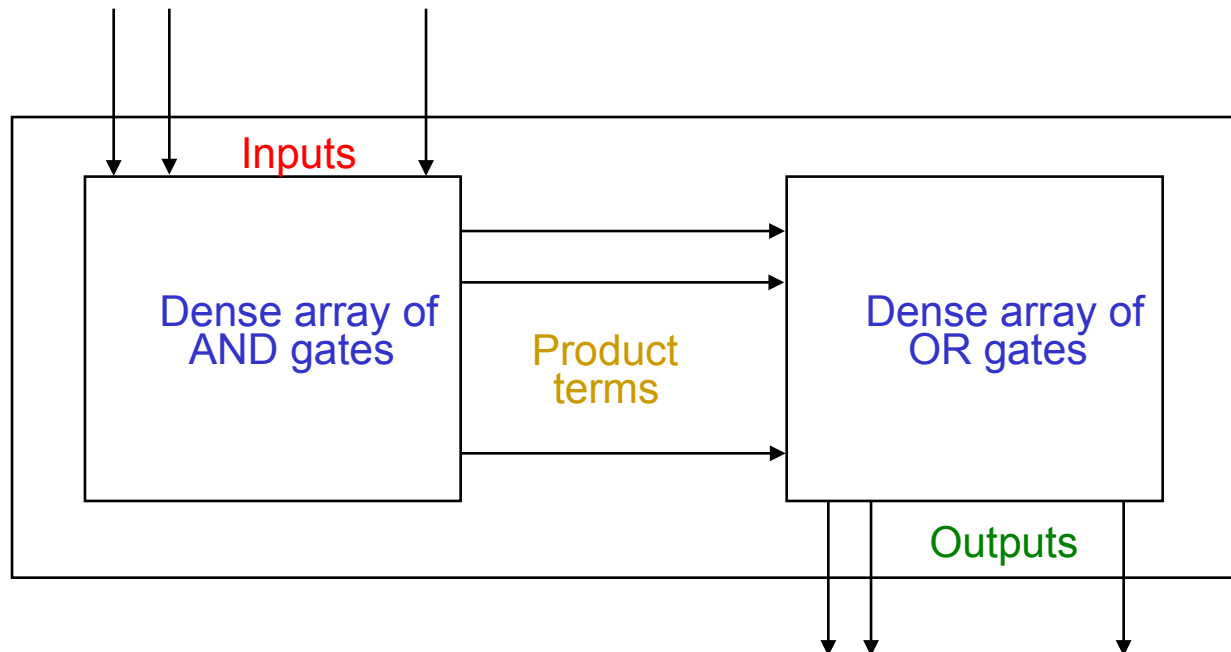

Programmable Logic

PROGRAMMABLE LOGIC DEVICES (PLDs)

PROM	Programmable Read-Only Memory Fixed "AND" array with 2^n (# Inputs) minterms Programmable "OR" array with m output bits
EPROM	Erasable PROM Erase with ultraviolet light, and program again
EEPROM	Electrically Erasable PROM Erase addressed byte with 20 volts
Flash Memory	High density, low cost EEPROM Non-selective complete erase with 20 volts
PAL	Programmable Array Logic Programmable "AND" array with n product terms Fixed "OR" array, each of m outputs has n/m terms
PLA	Programmable Logic Array Programmable "AND" array with n product terms Programmable "OR" array with m output bits
PLS	Programmable Logic Sequencer PLA plus Flip-Flops and extra combinational logic
FPGA	Field Programmable Gate Array Dynamically configurable logic and I/O blocks

Programmable Logic Organization

- Pre-fabricated building block of many AND/OR gates (or NOR, NAND)
- "Personalized" by making or breaking connections among the gates



Programmable Array Block Diagram for Sum of Products Form

Basic Programmable Logic Organizations

- Depending on which of the AND/OR logic arrays is programmable, we have three basic organizations

ORGANIZATION	AND ARRAY	OR ARRAY
PAL	PROG.	FIXED
PROM	FIXED	PROG.
PLA	PROG.	PROG.

 
 
 


Fig. 7-13 Basic Configuration of Three PLDs

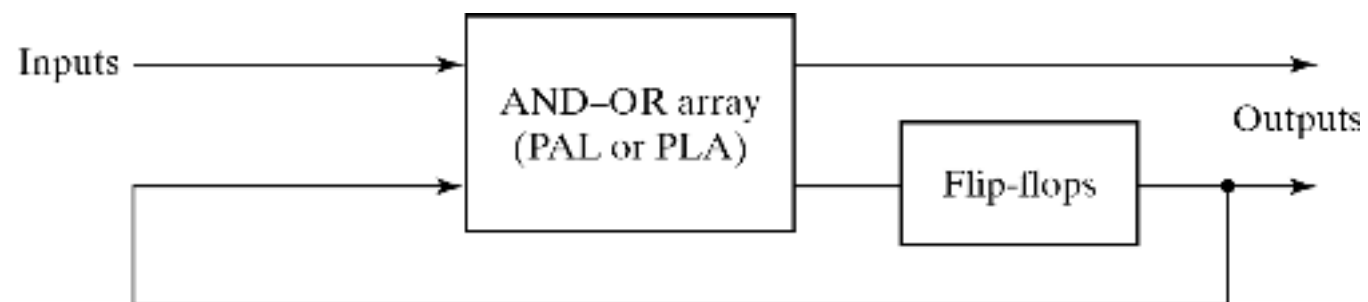


Fig. 7-18 Sequential Programmable Logic Device

PLA Logic Implementation

Key to Success: Shared Product Terms

Equations

Example:

$$\begin{aligned} F_0 &= A + \bar{B} \bar{C} \\ F_1 &= A \bar{C} + A B \\ F_2 &= \bar{B} \bar{C} + A B \\ F_3 &= \bar{B} C + A \end{aligned}$$

Personality Matrix

Product term	Inputs			Outputs			
	A	B	C	F ₀	F ₁	F ₂	F ₃
A B	1	1	-	0	①	①	0
$\bar{B} C$	-	0	1	0	0	0	①
A \bar{C}	1	-	0	0	①	0	0
$\bar{B} \bar{C}$	-	0	0	①	0	①	0
A	1	-	-	①	0	0	①

Input Side:


1 = asserted in term
 0 = negated in term
 - = does not participate

Output Side:

1 = term connected to output
 0 = no connection to output

PLA Logic Implementation

Example Continued - Unprogrammed device

 

PLA Table Generation

$$F_1 = AB' + C$$


$$F_2 = A'C' + BC$$

$$F_3 = AB' + A'C'$$


$$F_4 = A'C' + BC + AB'C$$

Product Term	Input (Actual)						Input (Specified)			Outputs			
	A	A'	B	B'	C	C'	A	B	C	F ₁	F ₂	F ₃	F ₄
AB'	1	0	0	1	0	0	1	0	-	1	0	1	0
C	0	0	0	0	1	0	-	-	1	1	0	0	0
A'C'	0	1	0	0	0	1	0	-	0	0	1	1	1
BC	0	0	1	0	1	0	-	1	1	0	1	0	1
AB'C	1	0	0	1	1	0	1	0	1	0	0	0	1


Internal PLA Structure

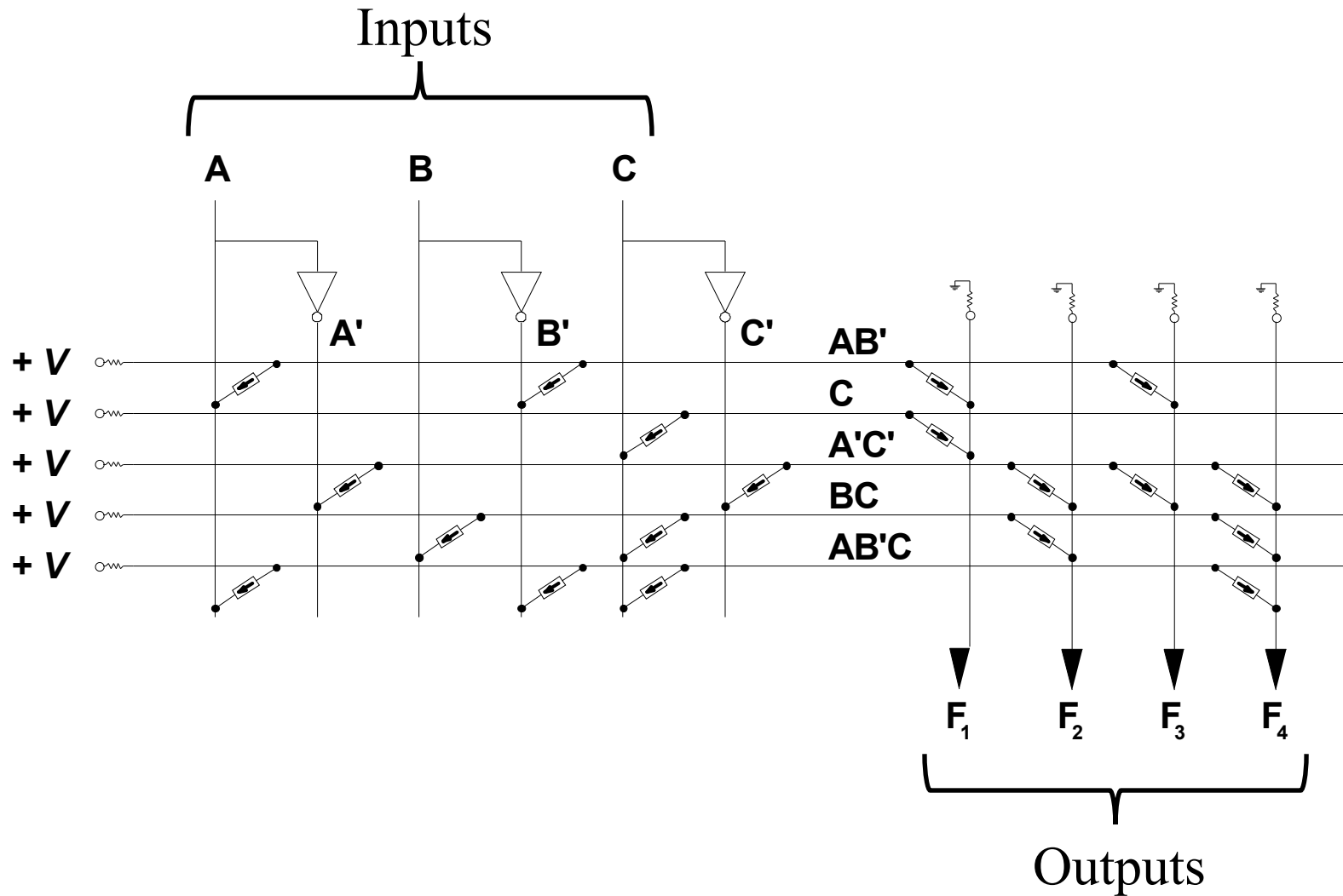

Internal PLA Structure

 


Internal PLA Structure

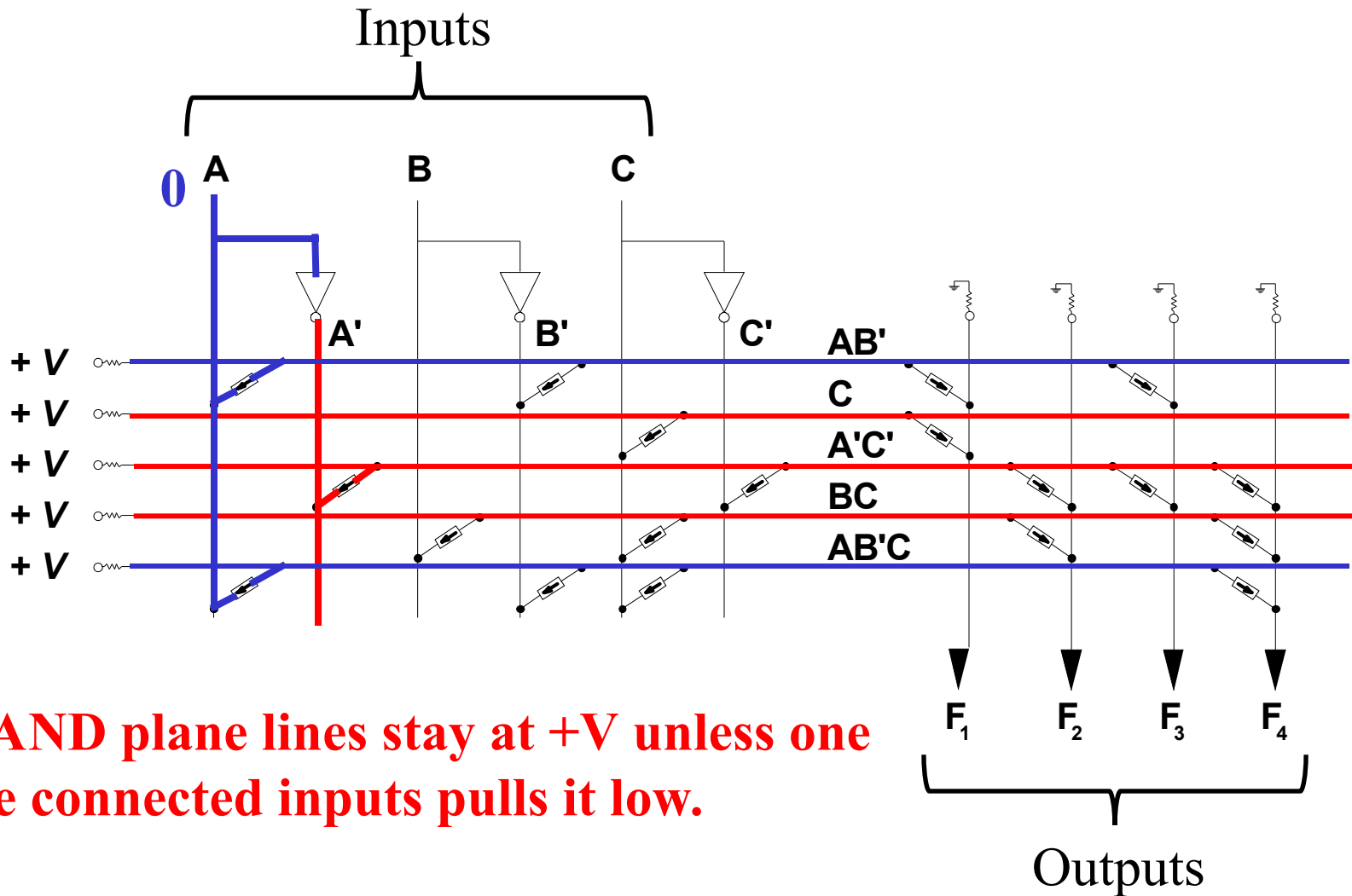


The AND plane lines stay at +V unless one of the connected inputs pulls it low.

Internal PLA Structure

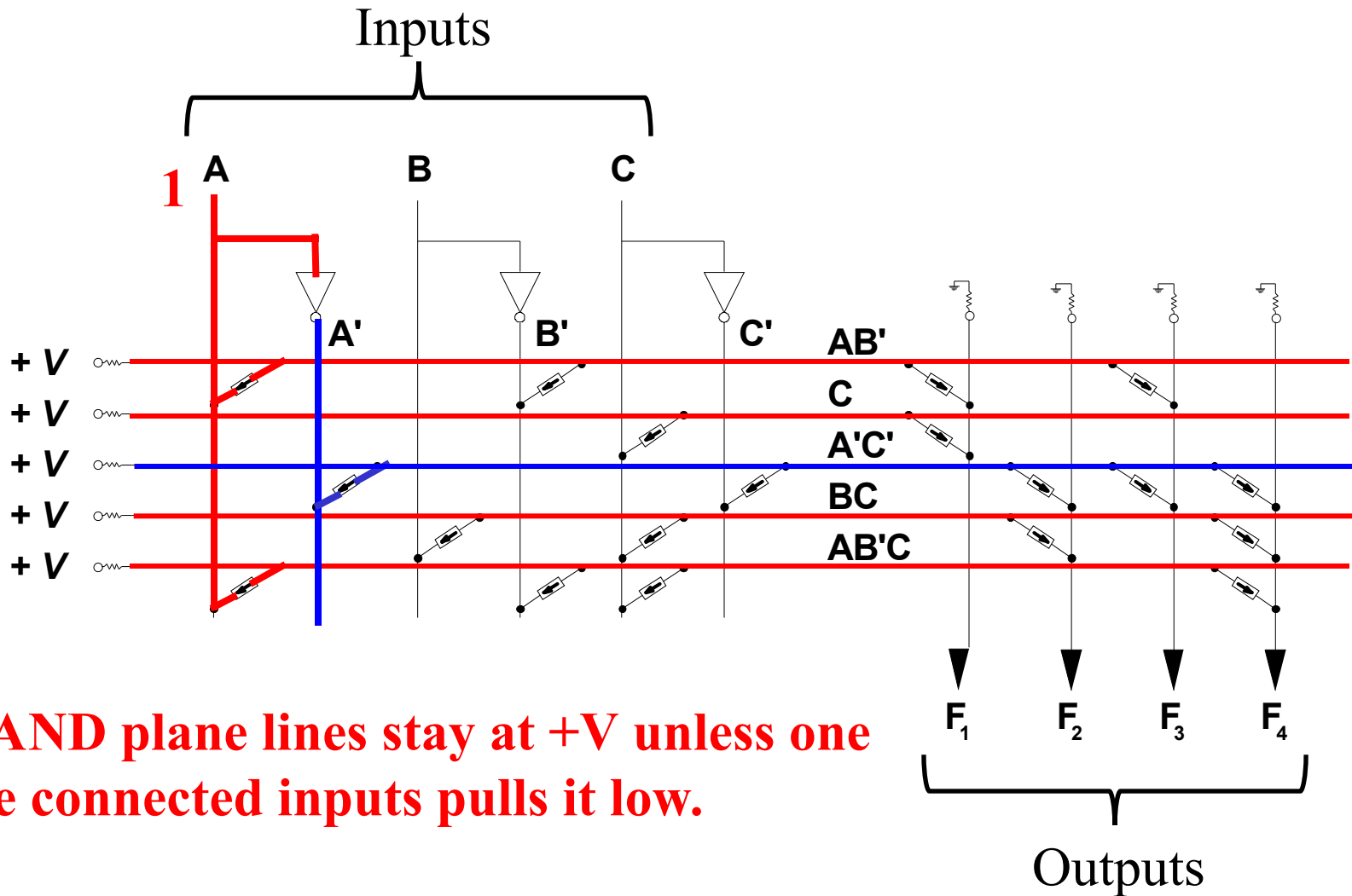


The AND plane lines stay at +V unless one of the connected inputs pulls it low.

Internal PLA Structure

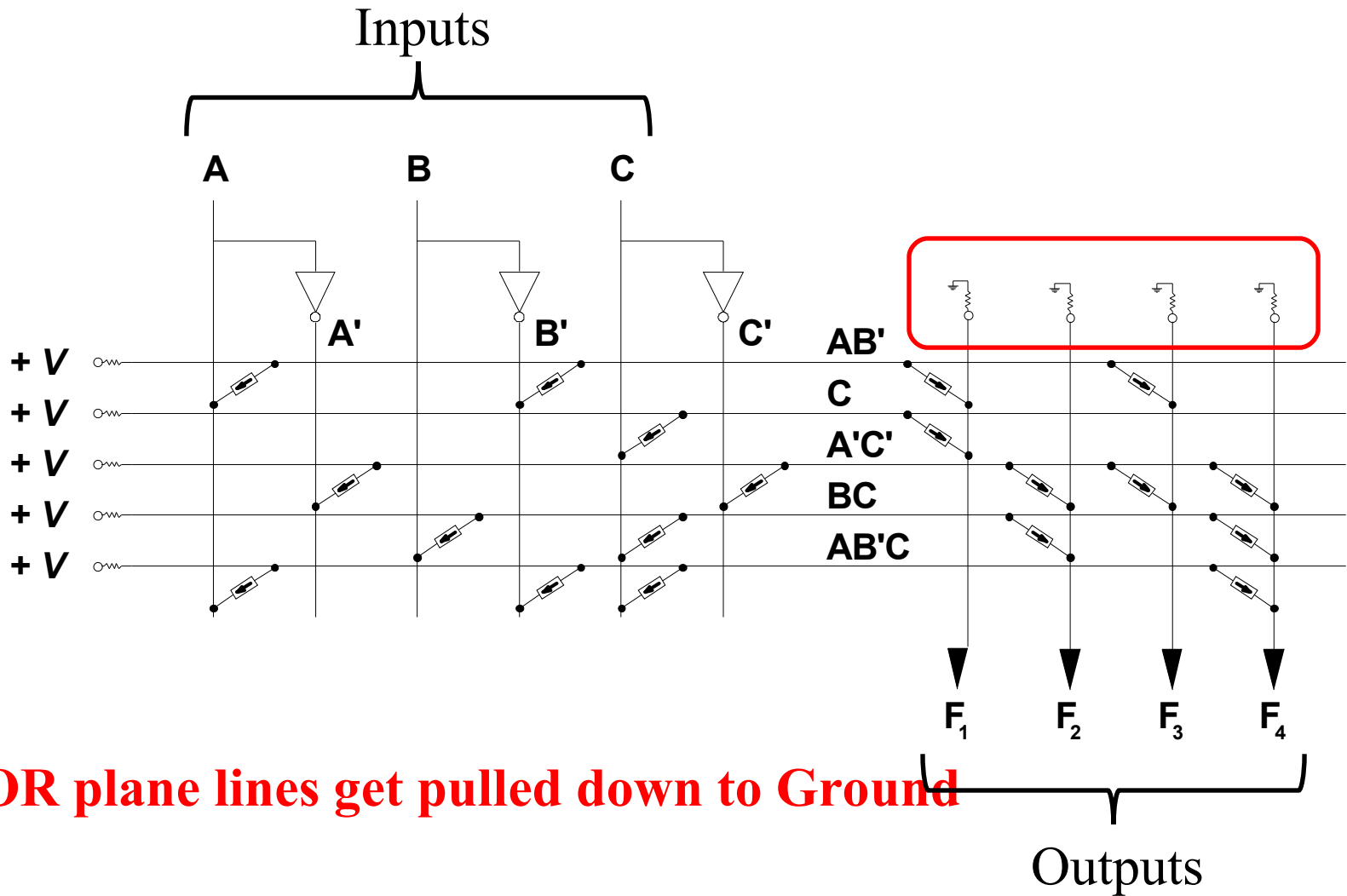


The OR plane lines get pulled down to Ground

Internal PLA Structure

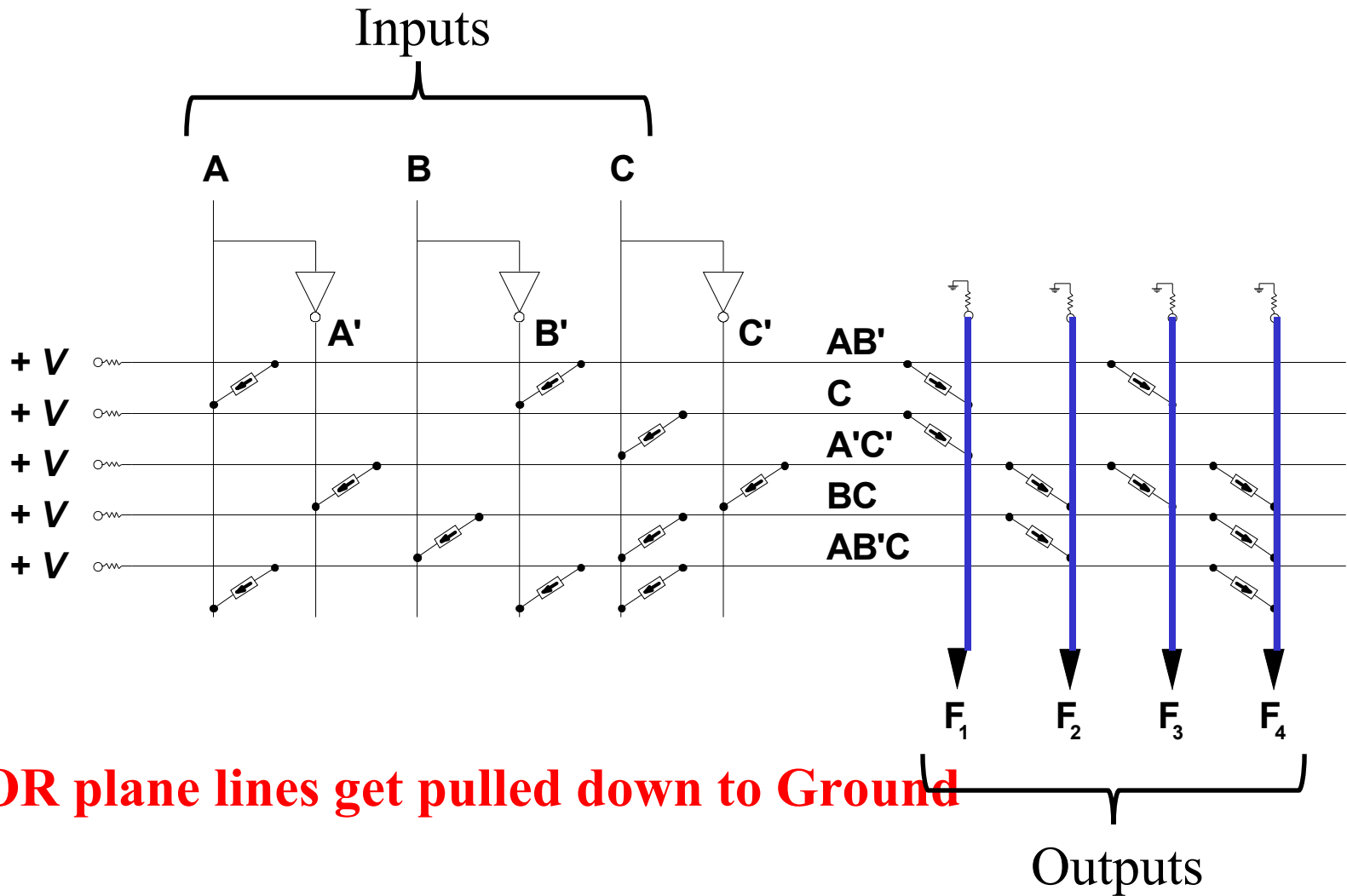


Internal PLA Structure

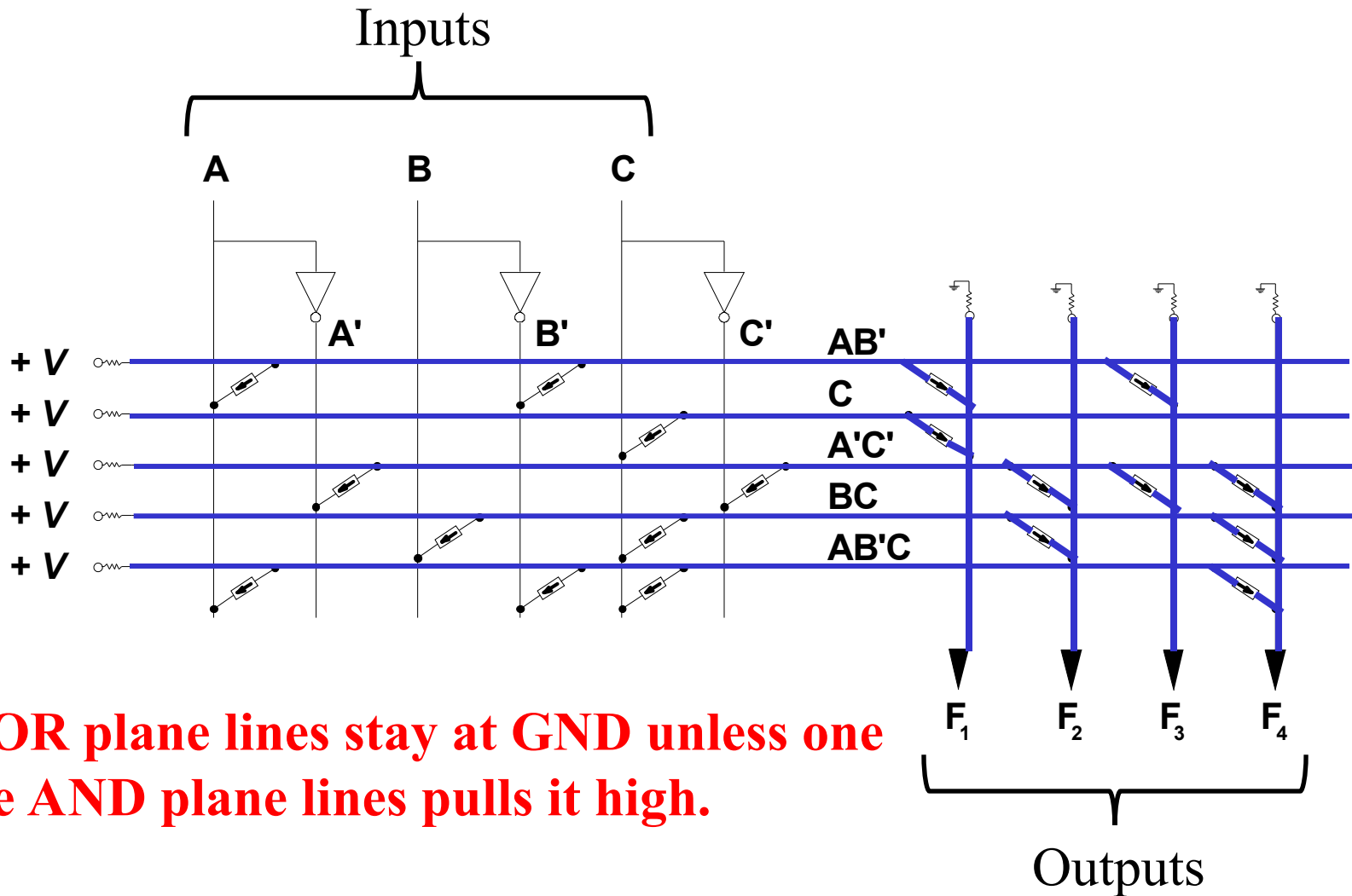


The OR plane lines stay at GND unless one of the AND plane lines pulls it high.

Internal PLA Structure

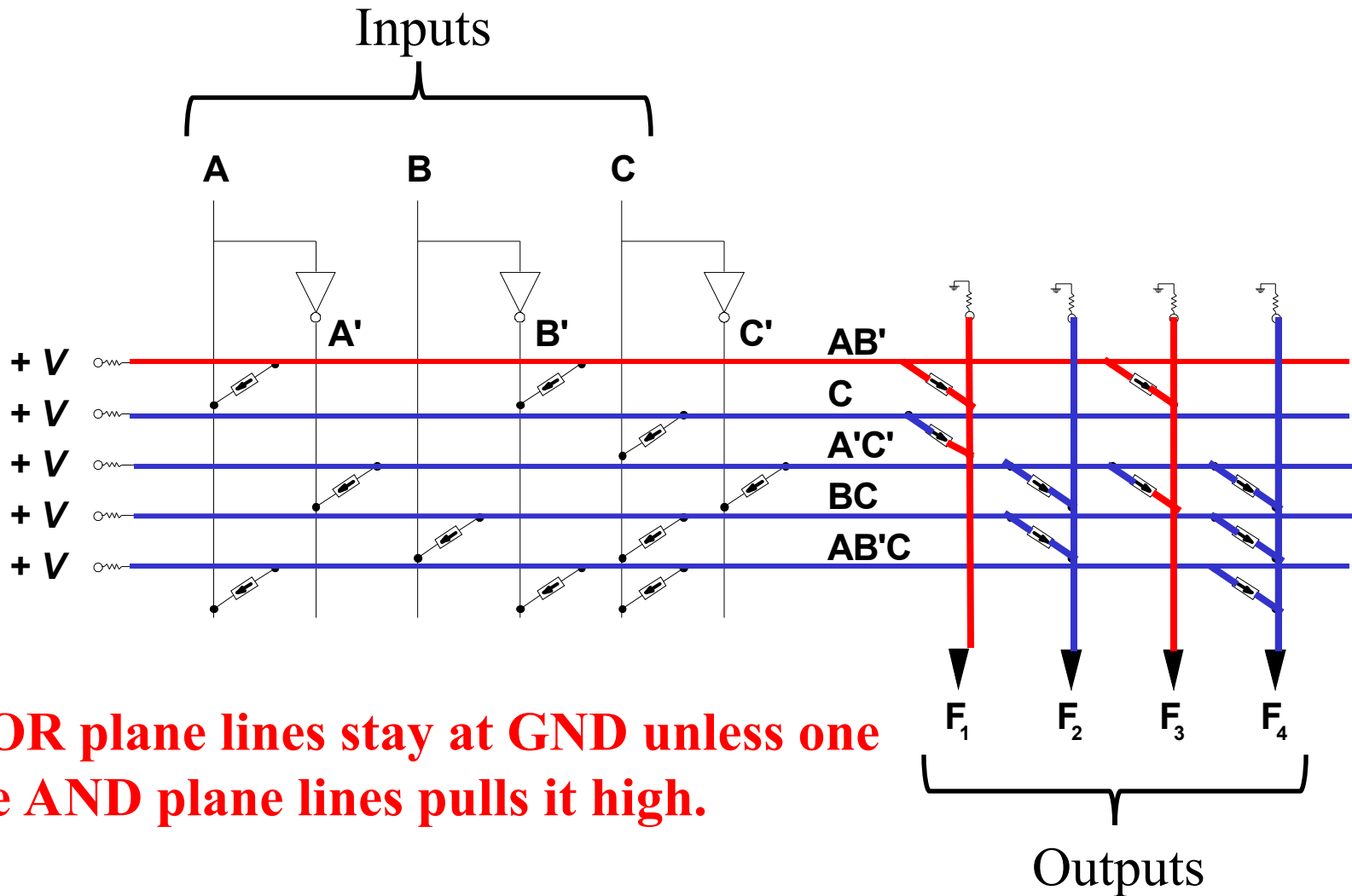


Internal PLA Structure

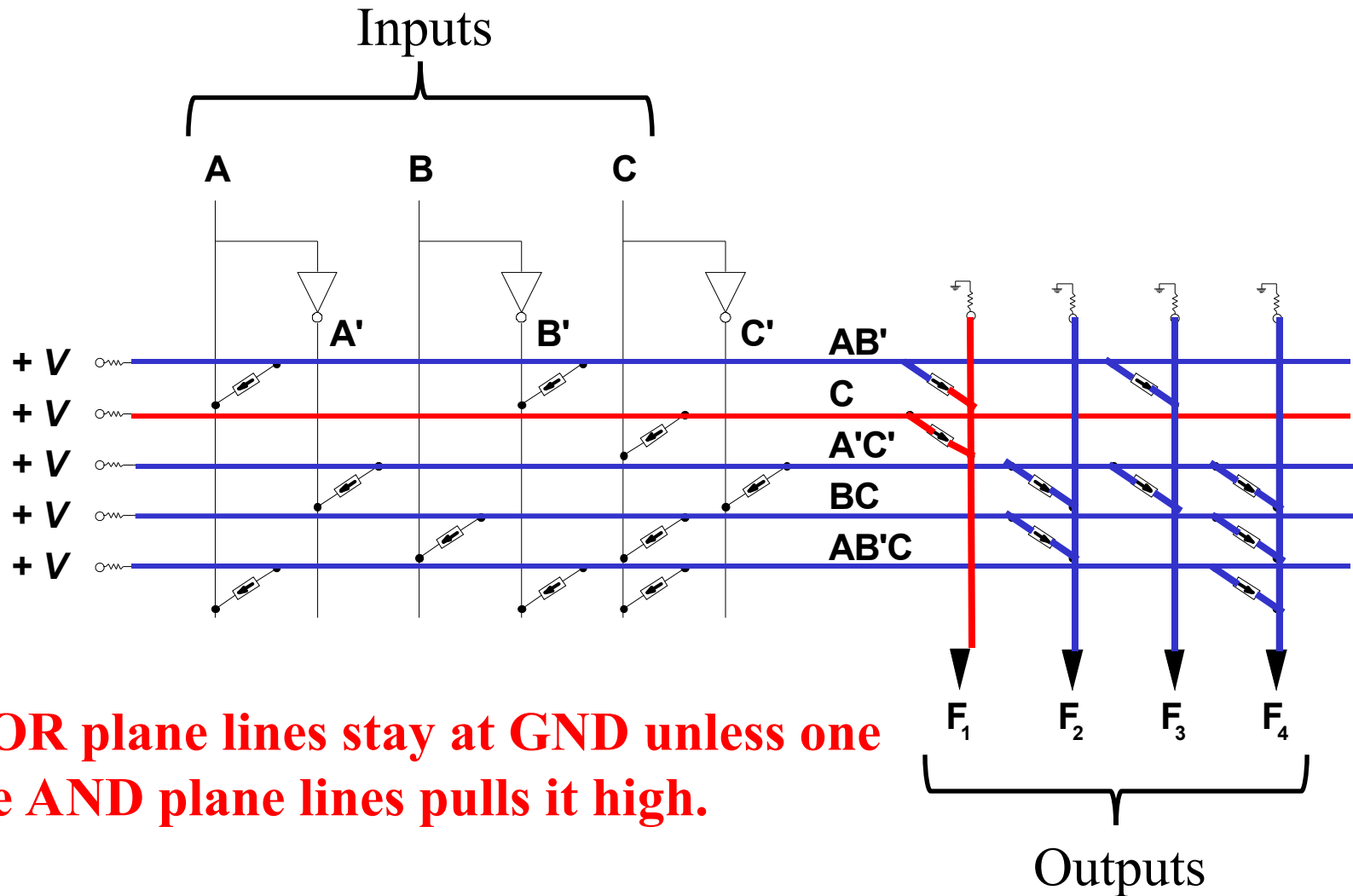

The OR plane lines stay at GND unless one of the AND plane lines pulls it high.


Internal PLA Structure

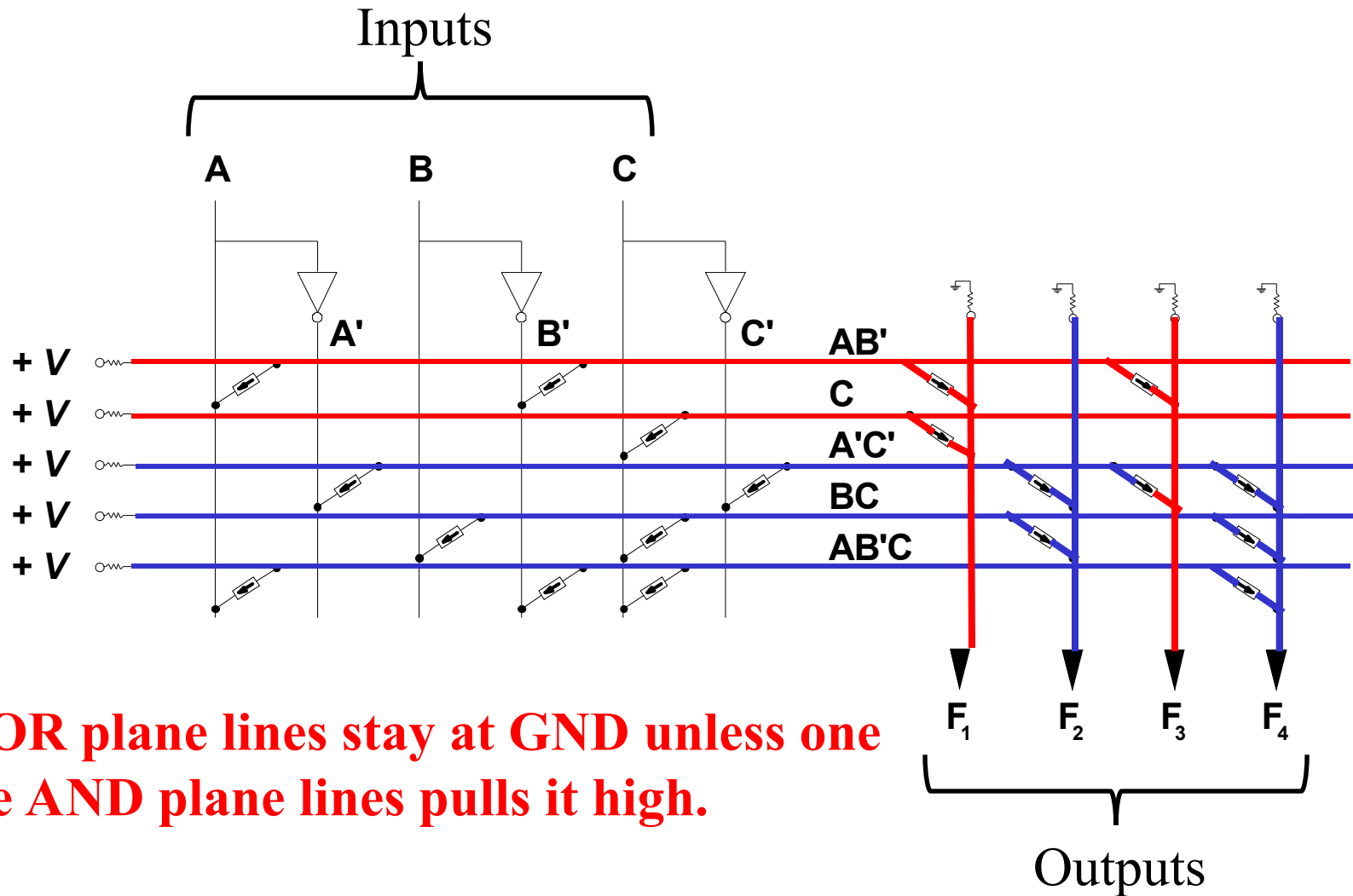

The OR plane lines stay at GND unless one of the AND plane lines pulls it high.

PLA Logic Implementation

**Example Continued -
Programmed part**

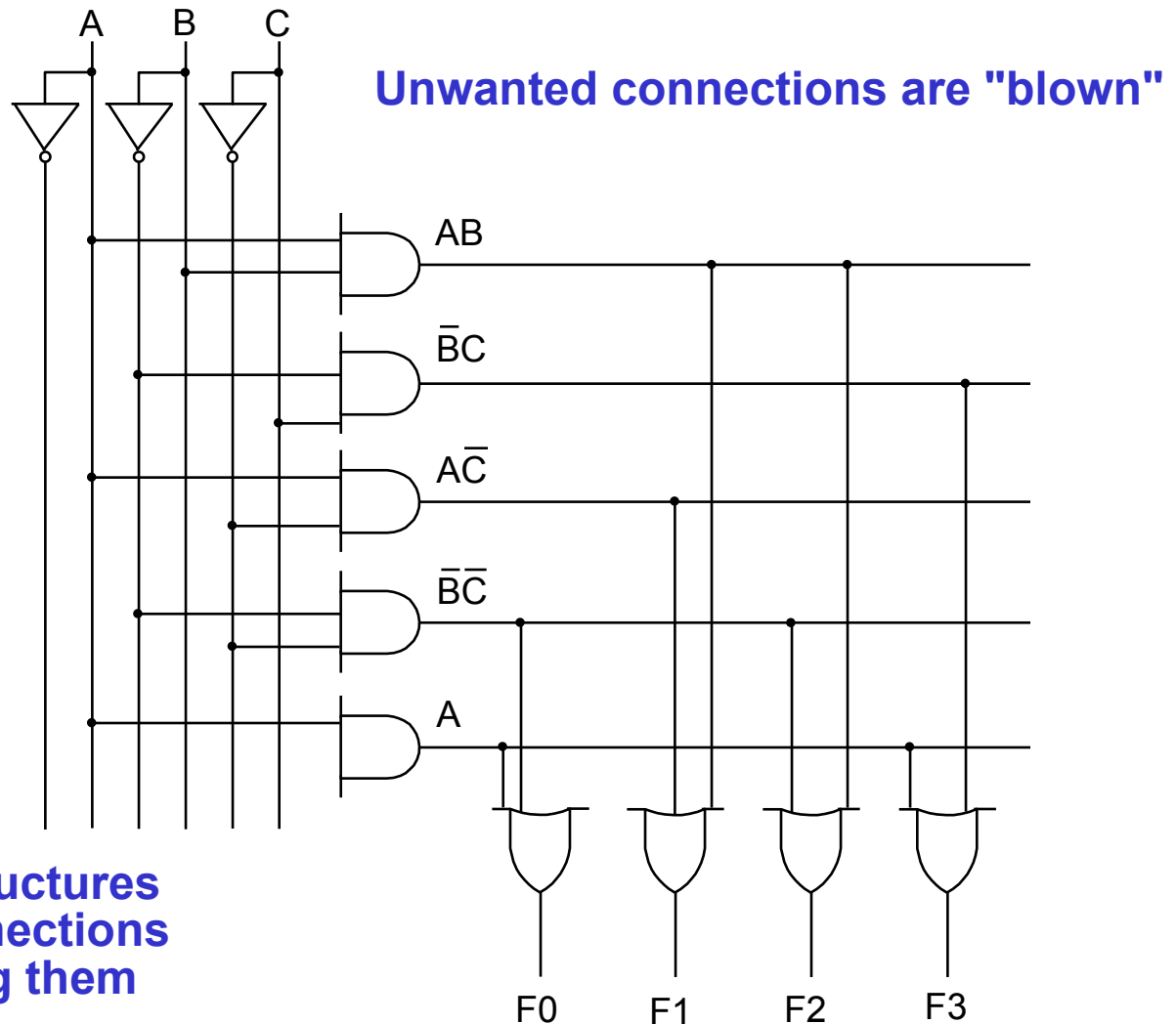

PLA Logic Implementation

Alternative representation for high fan-in structures


Short-hand notation so we don't have to draw all the wires!

X at junction indicates a connection

Notation for implementing

$$F0 = A B + \bar{A} \bar{B}$$

$$F1 = C \bar{D} + \bar{C} D$$

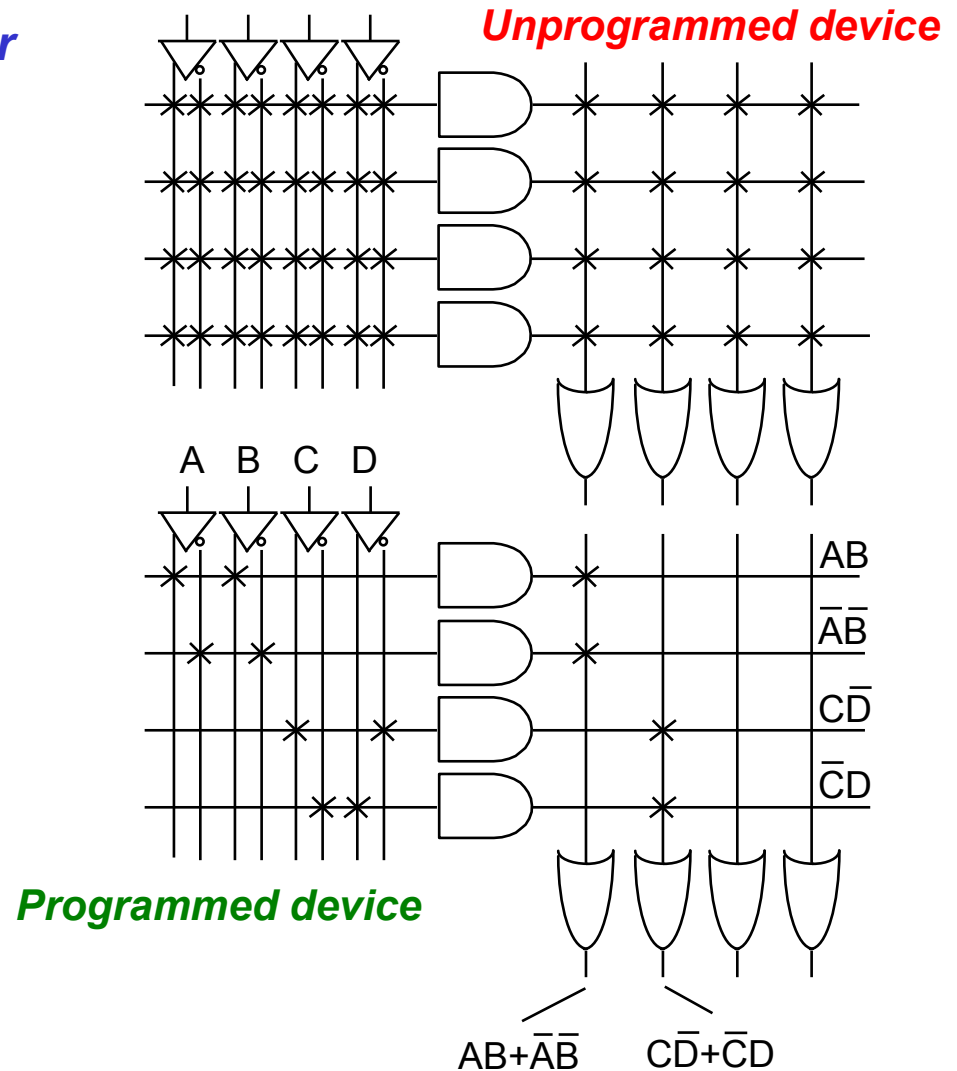

PLA Logic Implementation

Design Example

Multiple functions of A, B, C

$$F1 = A B C$$


$$F2 = A + B + C$$

$$F3 = \overline{A B C}$$

$$F4 = \overline{A + B + C}$$






$$F5 = A \oplus B \oplus C$$

$$F6 = \overline{A \oplus B \oplus C}$$

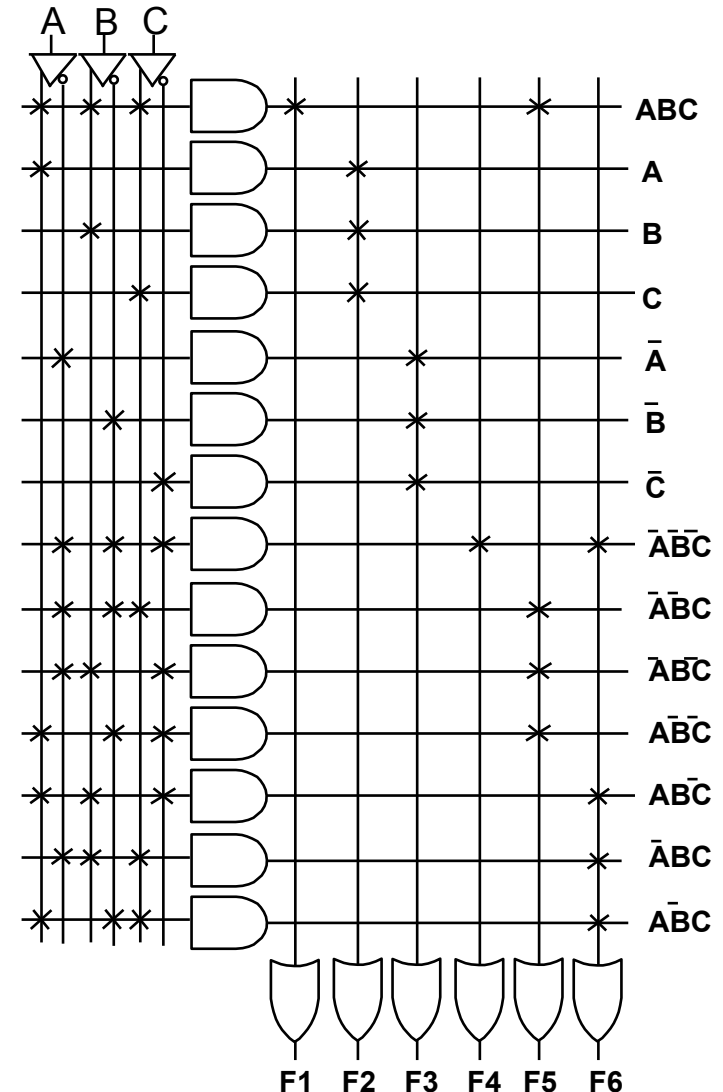


PLA Logic Implementation

Another Example: Magnitude Comparator

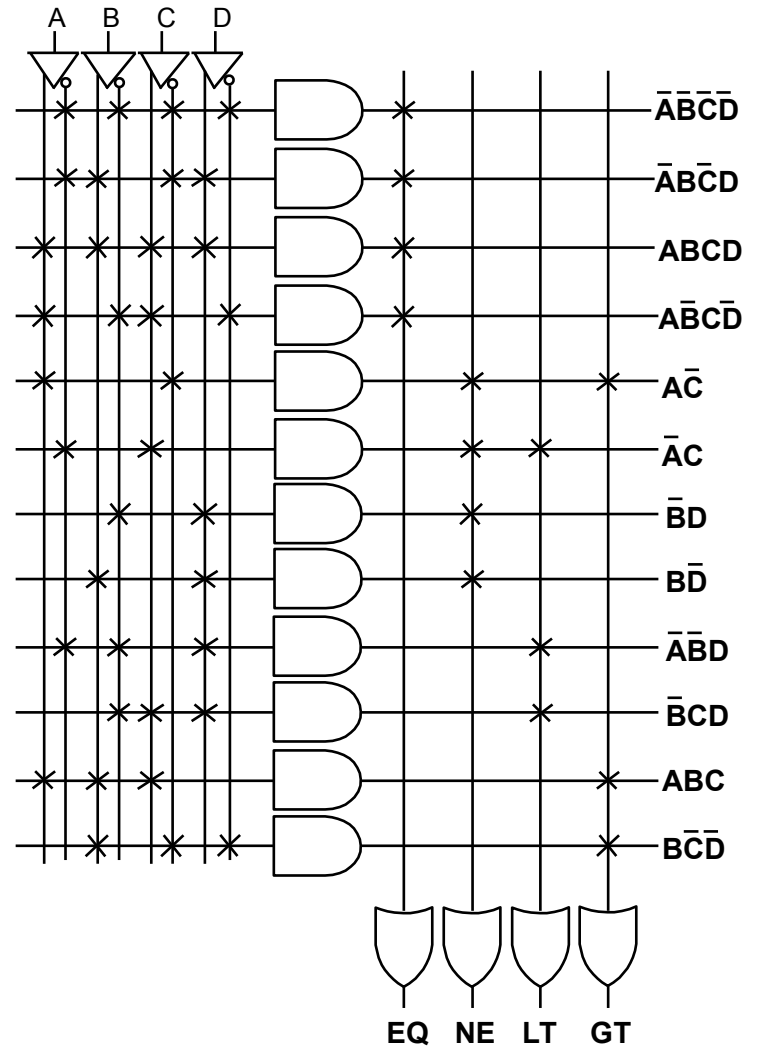    

Another PLA Representation

 

PLA Example

Implement these equations:


$$X = ABC^1 + B'^2D'^3 + AB'^3D + C'^4D'$$

$$Y = BC^5 + D'^6$$

8 terms

$$Z = CD^7 + B'^2D'^3 + A'^8BC$$

in this PLA:

 

can we implement 8 product terms with 6 AND plane lines?

PLA Example

Implement these equations:

$$X = ABC + B'D' + AB'D + C'D'$$

$$Y = BC + D'$$

$$Z = CD + B'D' + A'BC$$

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		X			
		00	01	11	10
00					
01					
11					
10					

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		Y			
		00	01	11	10
00					
01					
11					
10					

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		Z			
		00	01	11	10
00					
01					
11					
10					

PLA Example

Implement these equations:

$$X = ABC + B'D' + AB'D + C'D'$$

$$Y = BC + D'$$

$$Z = CD + B'D' + A'BC$$

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		X			
		00	01	11	10
00		1	1	1	1
01					1
11				1	1
10		1		1	1

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		Y			
		00	01	11	10
00					
01					
11					
10					

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		Z			
		00	01	11	10
00					
01					
11					
10					

PLA Example

Implement these equations:

$$X = ABC + B'D' + AB'D + C'D'$$

$$Y = BC + D'$$

$$Z = CD + B'D' + A'BC$$

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		X			
		00	01	11	10
00		1	1	1	1
01					1
11				1	1
10		1		1	1

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		Y			
		00	01	11	10
00		1	1	1	1
01					
11			1	1	
10		1	1	1	1

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		Z			
		00	01	11	10
00					
01					
11					
10					

PLA Example

Implement these equations:

$$X = ABC + B'D' + AB'D + C'D'$$

$$Y = BC + D'$$

$$Z = CD + B'D' + A'BC$$

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		X			
		00	01	11	10
00		1	1	1	1
01					1
11				1	1
10		1		1	1

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		Y			
		00	01	11	10
00		1	1	1	1
01					
11			1	1	
10		1	1	1	1

$\begin{array}{c} A \ B \\ \hline C \ D \end{array}$		Z			
		00	01	11	10
00		1			1
01					
11		1	1	1	1
10		1	1		1

PLA Example

$C'D'$ is in **X** and **Y** and looks useful

		X			
		00	01	11	10
C D	00	1	1	1	1
	01				1
	11			1	1
	10	1		1	1

		Y			
		00	01	11	10
C D	00	1	1	1	1
	01				
	11		1	1	
	10	1	1	1	1

		Z			
		00	01	11	10
C D	00	1			1
	01				
	11	1	1	1	1
	10	1	1		1

PLA Example

$C'D'$ is in **X** and **Y** and looks useful

$B'D'$ is in all three functions

		X			
		00	01	11	10
C D	00	1	1	1	1
	01				1
	11			1	1
	10	1		1	1

		Y			
		00	01	11	10
C D	00	1	1	1	1
	01				
	11		1	1	
	10	1	1	1	1

		Z			
		00	01	11	10
C D	00	1			1
	01				
	11	1	1	1	1
	10	1	1		1

PLA Example

$C'D'$ is in **X** and **Y** and looks useful

$B'D'$ is in all three functions

$A'BC$ and **ABC** cover a lot of minterms

		X			
		00	01	11	10
C D	00	1	1	1	1
	01				1
	11			1	1
	10	1		1	1

		Y			
		00	01	11	10
C D	00	1	1	1	1
	01				
	11		1	1	
	10	1	1	1	1

		Z			
		00	01	11	10
C D	00	1			1
	01				
	11	1	1	1	1
	10	1	1		1

PLA Example

$C'D'$ is in **X** and **Y** and looks useful

B'D' is in all three functions

A'BC and **ABC** cover a lot of minterms

		X			
A B		00	01	11	10
C D	00	1	1	1	1
	01				1
	11			1	1
	10	1		1	1

		Y			
A B		00	01	11	10
C D	00	1	1	1	1
	01				
	11		1	1	
	10	1	1	1	1

		Z			
A B		00	01	11	10
C D	00	1			1
	01				
	11	1	1	1	1
	10	1	1		1

The only ones left are AB' and CD

PLA Example

$$X = C'D' + B'D' + AB' + ABC$$

$$Y = C'D' + B'D' + ABC + A'BC$$

$$Z = B'D' + CD + A'BC$$

All of the functions are covered using only 6 product terms

A B \ C D		X			
		00	01	11	10
00	1	1	1	1	
01				1	
11			1	1	
10	1		1	1	

A B		Y			
		00	01	11	10
C D					
00	1	1	1	1	
01					
11		1	1		
10	1	1	1	1	

A B		Z			
		00	01	11	10
C D					
00	1				1
01					
11	1	1	1	1	
10	1	1		1	

How is this possible?

PLA Example

$$X = C'D' + B'D' + AB' + ABC$$

$$Y = C'D' + B'D' + ABC + A'BC$$

$$Z = B'D' + CD + A'BC$$

Product Term	Input				Output		
	A	B	C	D	X	Y	Z
C'D'							
B'D'							
AB'							
ABC							
A'BC							
CD							

PLA Example

$$X = C'D' + B'D' + AB' + ABC$$

$$Y = C'D' + B'D' + ABC + A'BC$$

$$Z = B'D' + CD + A'BC$$

Product Term	Input				Output		
	A	B	C	D	X	Y	Z
C'D'	-	-	0	0			
B'D'	-	0	-	0			
AB'	1	0	-	-			
ABC	1	1	1	-			
A'BC	0	1	1	-			
CD	-	-	1	1			

PLA Example

$$X = C'D' + B'D' + AB' + ABC$$

$$Y = C'D' + B'D' + ABC + A'BC$$

$$Z = B'D' + CD + A'BC$$

Product Term	Input				Output		
	A	B	C	D	X	Y	Z
C'D'	-	-	0	0	1	1	0
B'D'	-	0	-	0	1	1	1
AB'	1	0	-	-	1	0	0
ABC	1	1	1	-	1	1	0
A'BC	0	1	1	-	0	1	1
CD	-	-	1	1	0	0	1


PLA Example

$$X = C'D' + B'D' + AB' + ABC$$

$$Y = C'D' + B'D' + ABC + A'BC$$

$$Z = B'D' + CD + A'BC$$

Product Term	Input				Output		
	A	B	C	D	X	Y	Z
C'D'	-	-	0	0	1	1	0
B'D'	-	0	-	0	1	1	1
AB'	1	0	-	-	1	0	0
ABC	1	1	1	-	1	1	0
A'BC	0	1	1	-	0	1	1
CD	-	-	1	1	0	0	1

 


PALs and

PLAs

What is difference between Programmable Array Logic (PAL) and Programmable Logic Array (PLA)?

 PAL concept — implemented by Monolithic Memories
AND array is programmable, OR array is fixed at fabrication



A given column of the OR array has access to only a subset of the possible product terms

PLA concept — Both AND and OR arrays are programmable

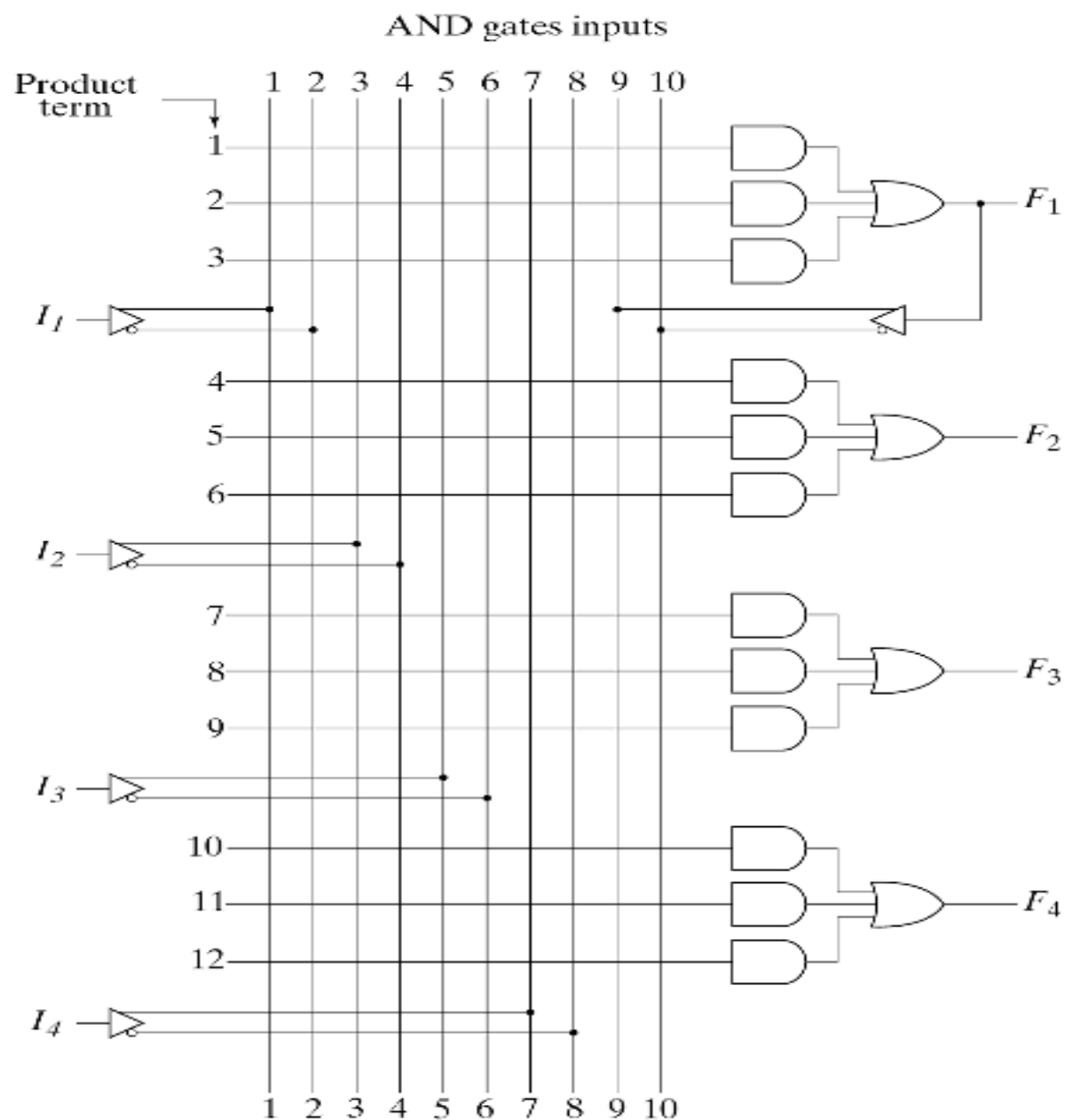


Fig. 7-16 PAL with Four Inputs, Four Outputs, and Three-Wide AND-OR Structure

$$X = A \bar{C} + B \bar{C} + \bar{B} C + \bar{B} D$$

$$Y = A C + A D + \bar{A} \bar{D} + \bar{B} \bar{C}$$

$$Z = A B + \bar{A} \bar{B}$$


$$X = A\bar{C} + B\bar{C} + \bar{B}(C+D)$$

$$Y = A(C+D) + \bar{A}\bar{D} + \bar{B}\bar{C}$$

$$Z = AB + \bar{A}\bar{B}$$

$$S = C + D$$

	AND Inputs					Output Function
	A	B	C	D	S	
1	-	-	1	-	-	$S = C + D$
2	-	-	-	1	-	
3	10	10	10	10	10	
4	1	-	0	-	-	$X = A\bar{C} + B\bar{C} + \bar{B}S$
5	-	1	0	-	-	
6	-	0	-	-	1	
7	1	-	-	-	1	$Y = AS + \bar{A}\bar{D} + \bar{B}\bar{C}$
8	0	-	-	0	-	
9	-	0	0	-	-	
10	1	1	-	-	-	$Z = AB + \bar{A}\bar{B}$
11	0	0	-	-	-	
12	10	10	10	10	10	

 

PALs and PLAs

- Of the two organizations the PLA is the most flexible
 - One PLA can implement a huge range of logic functions
 - BUT many pins; large package, higher cost
 - PALs are more restricted / you trade number of OR terms vs number of outputs
 - Many device variations needed
 - Each device is cheaper than a PLA
-

PAL Logic Implementation

Design Example: BCD to Gray Code Converter

K-maps

Truth Table

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X


Minimized Functions:

$$W = A + B\bar{D} + BC$$


$$X = B\bar{C}$$

$$Y = \bar{B} + C$$

 
$$Z = \bar{A}\bar{B}\bar{C}D + B\bar{C}D + A\bar{D} + \bar{B}C\bar{D}$$




K-map for W

 

K-map for X

 

K-map for Y

 

K-map for Z

PAL Logic Implementation

Programmed PAL:


Minimized Functions:

$$W = A + \bar{B}D + BC$$

$$X = B\bar{C}$$


$$Y = \bar{B} + \bar{C}$$
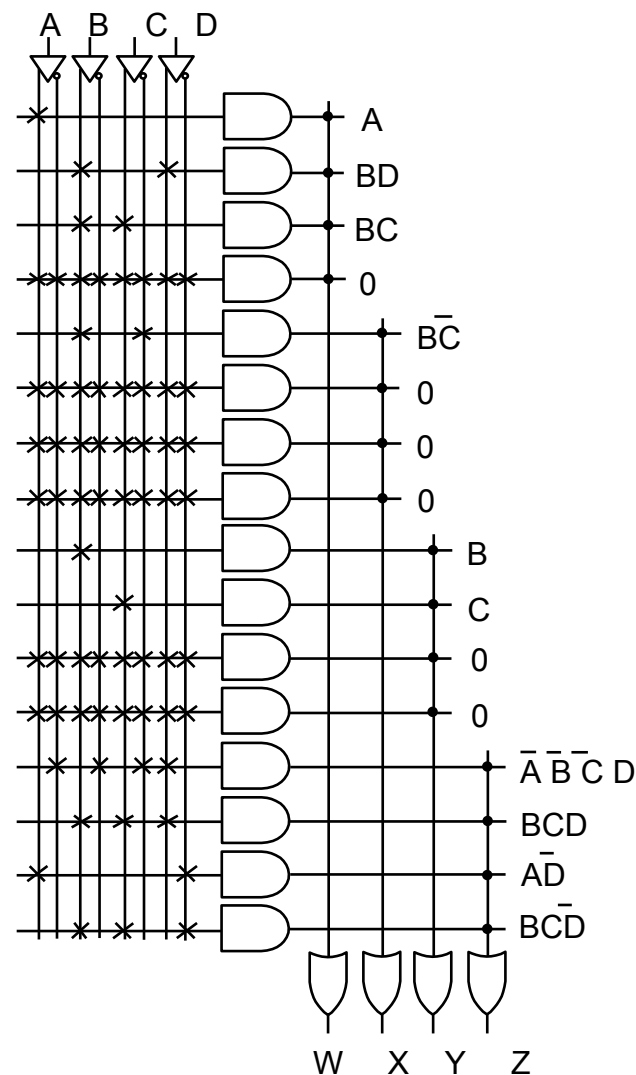
$$Z = \bar{A}\bar{B}\bar{C}D + BCD + A\bar{D} + \bar{B}C\bar{D}$$




4 product terms per each OR gate

PROM with 8 Words X 4 Bits

 

PLS with 2 Inputs and 3 Outputs

 


FPGA AND CPLD

1. FPGA - Field-Programmable Gate Array.
 2. CPLD - Complex Programmable Logic Device
 3. FPGA and CPLD is an advance PLD.
 4. Support thousands of gate where as PLD only support hundreds of gates.
-

What is an FPGA?

- Before the advent of programmable logic, custom logic circuits were built at the board level using standard components, or at the gate level in expensive application-specific (custom) integrated circuits.
- FPGA is an integrated circuit that contains many (64 to over 10,000) identical logic cells that can be viewed as standard components. Each logic cell can independently take on any one of a limited set of personalities.
- Individual cells are interconnected by a matrix of wires and programmable switches. A user's design is implemented by specifying the simple logic function for each cell and selectively closing the switches in the interconnect matrix.
- Array of logic cells and interconnect form a fabric of basic building blocks for logic circuits. Complex designs are created by combining these basic blocks to create the desired circuit

FPGA architecture

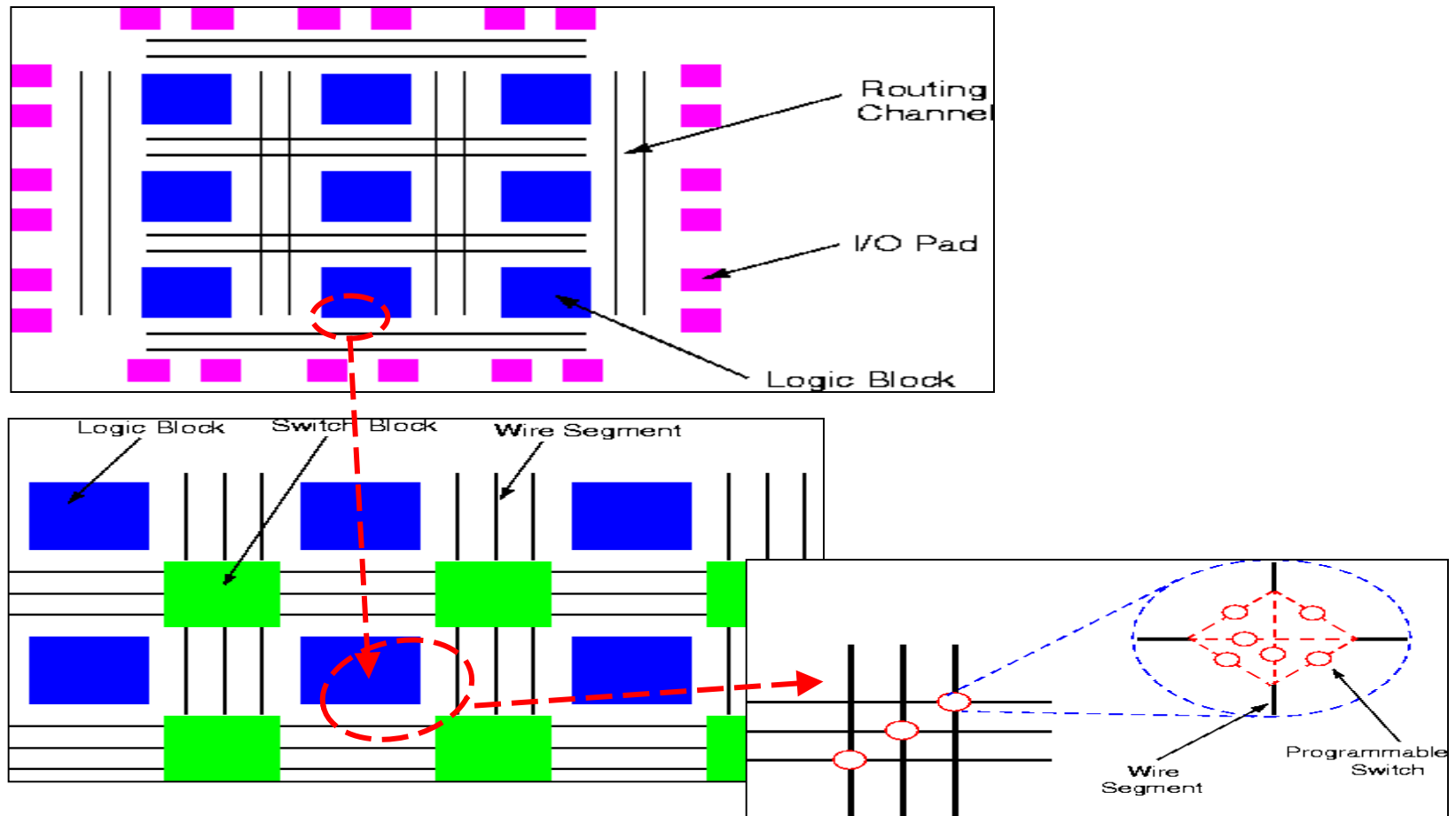

What does a logic cell do?

- The logic cell architecture varies between different device families.
- Each logic cell combines a few binary inputs (typically between 3 and 10) to one or two outputs according to a Boolean logic function specified in the user program .
- In most families, the user also has the option of registering the combinatorial output of the cell, so that clocked logic can be easily implemented.
- Cell's combinatorial logic may be physically implemented as a small look-up table memory (LUT) or as a set of multiplexers and gates.
- LUT devices tend to be a bit more flexible and provide more inputs per cell than multiplexer cells at the expense of propagation delay.

what does 'Field Programmable' mean?

- Field Programmable means that the FPGA's function is defined by a user's program rather than by the manufacturer of the device.
- A typical integrated circuit performs a particular function defined at the time of manufacture. In contrast, the FPGA's function is defined by a program written by someone other than the device manufacturer.
- Depending on the particular device, the program is either 'burned' in permanently or semi-permanently as part of a board assembly process, or is loaded from an external memory each time the device is powered up.
- This user programmability gives the user access to complex integrated designs without the high engineering costs associated with application specific integrated circuits.

How are FPGA programs created?

- Individually defining the many switch connections and cell logic functions would be a daunting task.
 - This task is handled by special software. The software translates a user's schematic diagrams or textual hardware description language code then places and routes the translated design.
 - Most of the software packages have hooks to allow the user to influence implementation, placement and routing to obtain better performance and utilization of the device.
 - Libraries of more complex function macros (eg. adders) further simplify the design process by providing common circuits that are already optimized for speed or area.
-

FPGA


- FPGA applications:-
 - i. DSP
 - ii. Software-defined radio
 - iii. Aerospace
 - iv. Defense system
 - v. ASIC Prototyping
 - vi. Medical Imaging
 - vii. Computer vision
 - viii. Speech Recognition
 - ix. Cryptography
 - x. Bioinformatic
 - xi. And others.

CPLD

1. Complexity of CPLD is between FPGA and PLD.
2. CPLD featured in common PLD:-
 - i. Non-volatile configuration memory – does not need an external configuration PROM.
 - ii. Routing constraints. Not for large and deeply layered logic.
3. CPLD featured in common FPGA:-
 - i. Large number of gates available.
 - ii. Can include complicated feedback path.
4. CPLD application:-
 - i. Address coding
 - ii. High performance control logic
 - iii. Complex finite state machines

CPLD

5. CPLD architecture:-

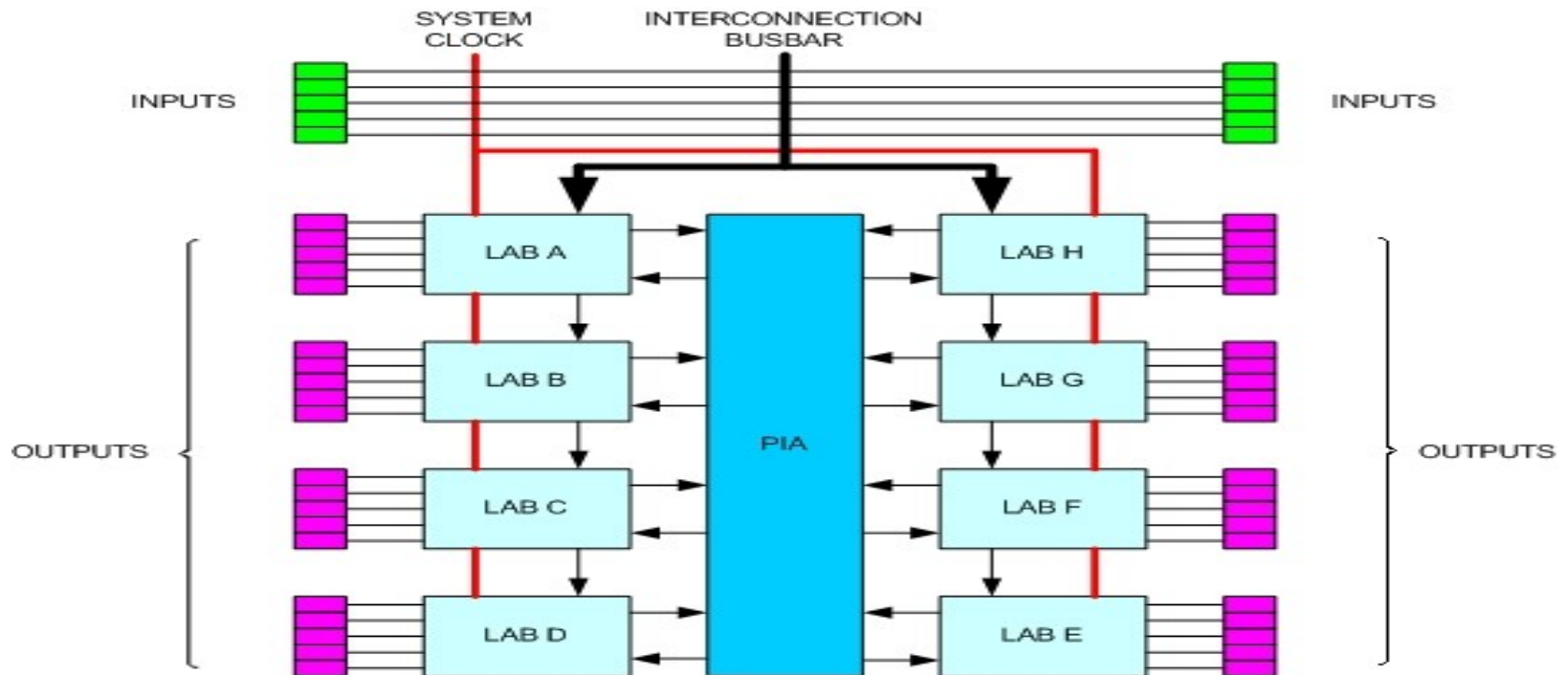

LAB – Logic Array Block / uses PALs

PIA – Programmable Interconnect Array