

# Gate-Level Minimization

## Bölüm 3

# 3-1 Introduction

- **Gate-level minimization** refers to the design task of finding an optimal gate-level implementation of Boolean functions describing a digital circuit.

# 3-2 The Map Method

- The complexity of the digital logic gates
  - The complexity of the algebraic expression
- Logic minimization
  - Algebraic approaches: lack specific rules
  - The Karnaugh map
    - A simple straight forward procedure
    - A pictorial form of a truth table
    - Applicable if the # of variables  $< 7$
- A diagram made up of squares
  - Each square represents one minterm

# Review of Boolean Function

## ■ Boolean function

- Sum of minterms
- Sum of products (or product of sum) in the simplest form
- A minimum number of terms
- A minimum number of literals
- The simplified expression may not be unique

# Two-Variable Map

- A two-variable map
  - Four minterms
  - $x' = \text{row } 0$ ;  $x = \text{row } 1$
  - $y' = \text{column } 0$ ;  $y = \text{column } 1$
  - A truth table in square diagram
  - Fig. 3.2(a):  $xy = m_3$
  - Fig. 3.2(b):  $x+y = x'y+xy' + xy = m_1+m_2+m_3$

 


Figure 3.1 Two-variable Map

 


Figure 3.2 Representation of functions in the map

# A Three-variable Map

- A three-variable map
  - Eight minterms
  - The Gray code sequence
  - Any two adjacent squares in the map differ by only one variable
    - Primed in one square and unprimed in the other
    - e.g.,  $m_5$  and  $m_7$  can be simplified
    - $m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

(a)

$x \backslash yz$				$y$	
		00	01	11	10
$x$	0	$m_0$ $x'y'z'$	$m_1$ $x'y'z$	$m_3$ $x'yz$	$m_2$ $x'yz'$
	1	$m_4$ $xy'z'$	$m_5$ $xy'z$	$m_7$ $xyz$	$m_6$ $xyz'$
		$z$			

(b)

Figure 3.3 Three-variable Map

# A Three-variable Map

- $m_0$  and  $m_2$  ( $m_4$  and  $m_6$ ) are adjacent
- $m_0 + m_2 = x'y'z' + x'yz' = x'z'(y' + y) = x'z'$
- $m_4 + m_6 = xy'z' + xyz' = xz'(y' + y) = xz'$

 


Fig. 3-3 Three-variable Map

# Example 3.1

- Example 3.1: simplify the Boolean function  $F(x, y, z) = \Sigma(2, 3, 4, 5)$ 
  - $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

 


Figure 3.4 Map for Example 3.1,  $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$



# Example 3.2

- Example 3.2: simplify  $F(x, y, z) = \Sigma(3, 4, 6, 7)$ 
  - $F(x, y, z) = \Sigma(3, 4, 6, 7) = yz + xz'$

 


Figure 3.5 Map for Example 3-2;  $F(x, y, z) = \Sigma(3, 4, 6, 7) = yz + xz'$

# Four adjacent Squares

- Consider four adjacent squares
  - 2, 4, and 8 squares
  - $m_0 + m_2 + m_4 + m_6 = x'y'z' + x'yz' + xy'z' + xyz' = x'z'(y' + y) + xz'(y' + y) = x'z' + xz' = z'$
  - $m_1 + m_3 + m_5 + m_7 = x'y'z + x'yz + xy'z + xyz = x'z(y' + y) + xz(y' + y) = x'z + xz = z$

 


Figure 3.3 Three-variable Map

# Example 3.3

■ Example 3.3: simplify  $F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$

■  $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$

 


Figure 3.6 Map for Example 3-3,  $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$

# Example 3.4

■ Example 3.4: let  $F = A'C + A'B + AB'C + BC$

a) Express it in sum of minterms.

b) Find the minimal sum of products expression.

Ans:

$$F(A, B, C) = \Sigma(1, 2, 3, 5, 7) = C + A'B$$

 


Figure 3.7 Map for Example 3.4,  $A'C + A'B + AB'C + BC = C + A'B$

# 3.3 Four-Variable Map

- The map
  - 16 minterms
  - Combinations of 2, 4, 8, and 16 adjacent squares


 


Figure 3.8 Four-variable Map

# Example 3.5

 - Example 3.5: simplify  $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$




$$F = y' + w'z' + xz'$$

Figure 3.9 Map for Example 3-5;  $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$

# Example 3.6

 - Example 3-6: simplify  $F = A'B'C' + B'CD' + A'B'C'D' + AB'C'$



Note:  $A'B'C'D' + A'B'CD' = A'B'D'$   
 $AB'C'D' + AB'CD' = AB'D'$   
 $A'B'D' + AB'D' = B'D'$   
 $A'B'C' + AB'C' = B'C'$

Figure 3.9 Map for Example 3-6;  $A'B'C' + B'CD' + A'B'C'D' + AB'C' = B'D' + B'C' + A'CD'$

# Prime Implicants



## ■ Prime Implicants

- All the minterms are covered.
- Minimize the number of terms.
- A prime implicant: a product term obtained by combining the maximum possible number of adjacent squares (combining all possible maximum numbers of squares).
- Essential P.I.: a minterm is covered by only one prime implicant.
- The essential P.I. must be included.


  
# Prime Implicants

- Consider  $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$ 
  - The simplified expression may not be unique
  - $F = BD + B'D' + CD + AD = BD + B'D' + CD + AB'$   
 $= BD + B'D' + B'C + AD = BD + B'D' + B'C + AB'$



# 3.4 Five-Variable Map

- Map for more than four variables becomes complicated
  - Five-variable map: two four-variable map (one on the top of the other).

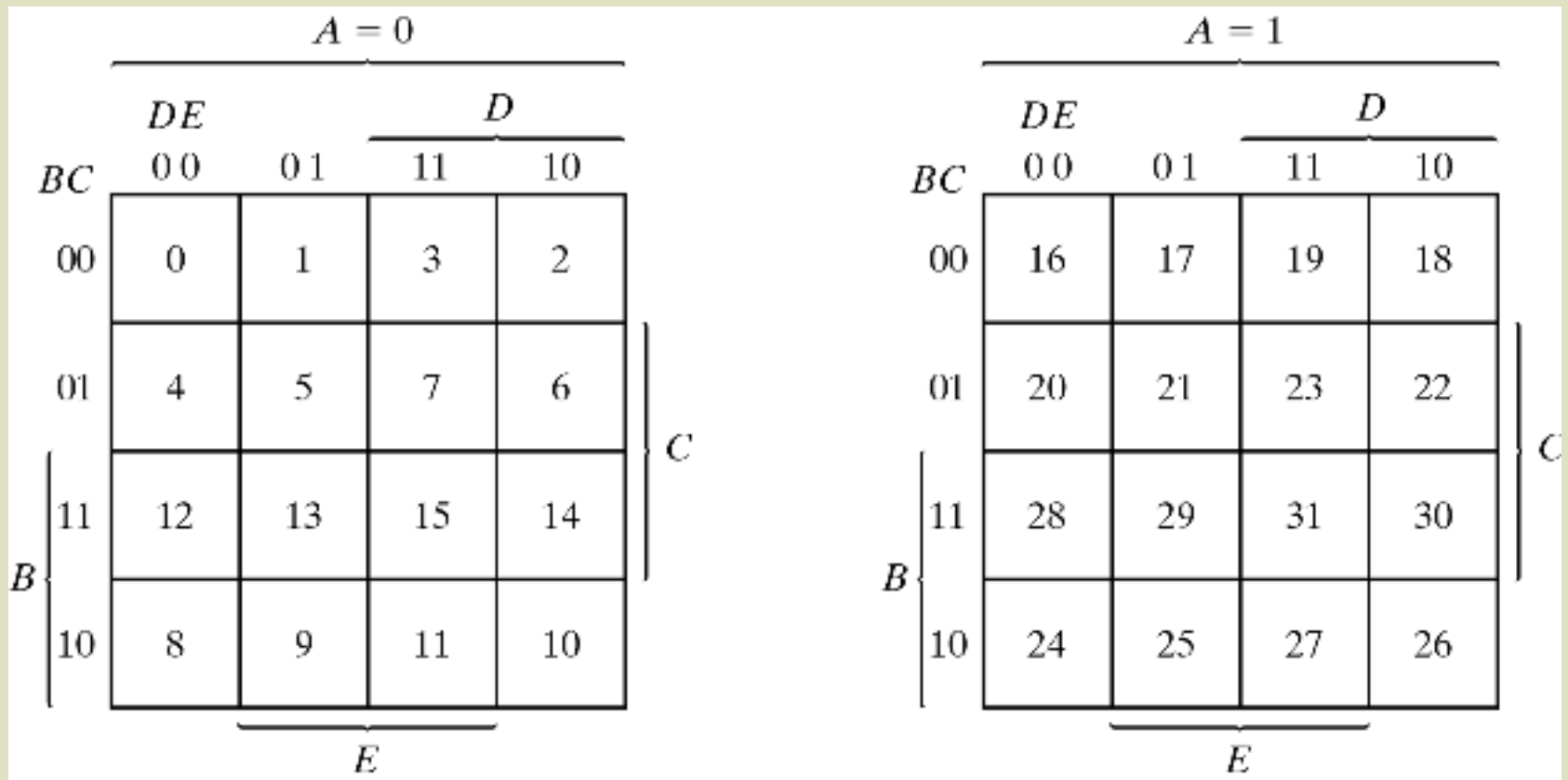


Figure 3.12 Five-variable Map

- Table 3.1 shows the relationship between the number of adjacent squares and the number of literals in the term.


**Table 3.1**

*The Relationship between the Number of Adjacent Squares and the Number of Literals in the Term*

<b><math>K</math></b>	<b>Number of Adjacent Squares <math>2^k</math></b>	<b>Number of Literals in a Term in an <math>n</math>-variable Map</b>			
		<b><math>n = 2</math></b>	<b><math>n = 3</math></b>	<b><math>n = 4</math></b>	<b><math>n = 5</math></b>
0	1	2	3	4	5
1	2	1	2	3	4
2	4	0	1	2	3
3	8		0	1	2
4	16			0	1
5	32				0

# Example 3.7

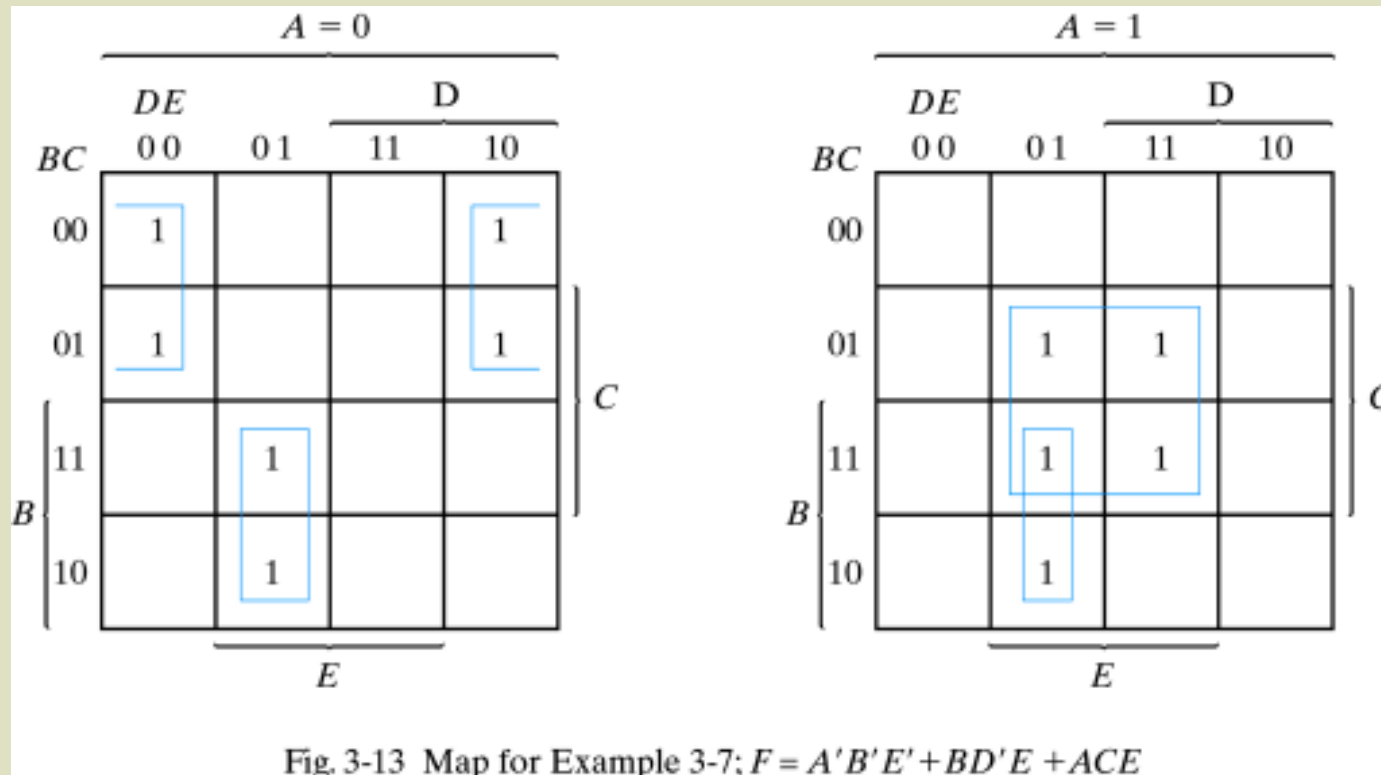- Example 3.7: simplify  $F = \Sigma(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$



$$F = A'B'E' + BD'E + ACE$$

# 3-5 Product of Sums Simplification

## ■ Approach #1

- Simplified  $F'$  in the form of sum of products
- Apply DeMorgan's theorem  $F = (F')'$
- $F'$ : sum of products  $\rightarrow F$ : product of sums


## ■ Approach #2: duality

- Combinations of maxterms (it was minterms)
- $M_0 M_1 = (A+B+C+D)(A+B+C+D') = (A+B+C)+(DD') = A+B+C$

AB \ CD	CD			
	00	01	11	10
00	$M_0$	$M_1$	$M_3$	$M_2$
01	$M_4$	$M_5$	$M_7$	$M_6$
11	$M_{12}$	$M_{13}$	$M_{15}$	$M_{14}$
10	$M_8$	$M_9$	$M_{11}$	$M_{10}$

# Example 3.8

 - Example 3.8: simplify  $F = \Sigma(0, 1, 2, 5, 8, 9, 10)$  into (a) sum-of-products form, and (b) product-of-sums form:



a)  $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D$


b)  $F' = AB + CD + BD'$

- » Apply DeMorgan's theorem;  
 $F = (A' + B')(C' + D')(B' + D)$
- » Or think in terms of maxterms


Figure 3.14 Map for Example 3.8,  $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D$
 
# Example 3.8 (cont.)

- Gate implementation of the function of Example 3.8



Sum-of products form

 

Product-of sums form

Figure 3.15 Gate Implementation of the Function of Example 3.8

# Sum-of-Minterm Procedure

- Consider the function defined in Table 3.2.
  - In sum-of-minterm:

$$F(x, y, z) = \sum(1, 3, 4, 6)$$

- $F(x, y, z) = x'z + xz'$
- In sum-of-maxterm:

$$F'(x, y, z) = \Pi(0, 2, 5, 7)$$

- $F'(x, y, z) = xz + x'z'$
- Taking the complement of  $F'$

$$F(x, y, z) = (x' + z')(x + z)$$

**Table 3.2**

*Truth Table of Function F*

<b>x</b>	<b>y</b>	<b>z</b>	<b>F</b>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0



# Sum-of-Minterm Procedure

- Consider the function defined in Table 3.2.
  - Combine the 1's:

$$F(x, y, z) = x'z + xz'$$

- Combine the 0's :

$$F'(x, y, z) = xz + x'z'$$

 


Figure 3.16 Map for the function of Table 3.2

# 3-6 Don't-Care Conditions

- The value of a function is not specified for certain combinations of variables
  - BCD; 1010-1111: don't care
- The don't-care conditions can be utilized in logic minimization
  - Can be implemented as 0 or 1
- Example 3.9: simplify  $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$  which has the don't-care conditions  $d(w, x, y, z) = \Sigma(0, 2, 5)$ .

# Example 3.9 (cont.)

- $F = yz + w'x'$ ;  $F = yz + w'z$
- $F = \Sigma(0, 1, 2, 3, 7, 11, 15)$ ;  $F = \Sigma(1, 3, 5, 7, 11, 15)$
- Either expression is acceptable

 


Figure 3.17 Example with don't-care Conditions

# TABLE METHOD (QUINN MC-CUSKEY)

- The expression is represented in the canonical SOP form (minterm form) if not already in that form.
- The function is converted into numeric notation.
- 
- The numbers are converted into binary form.
- The minterms are arranged in a column divided into groups.

Figure 3.17 Example with don't-care Conditions

# MINIMIZATION PROCEDURE

Each minterm of one group is compared with each minterm in the group immediately below.

Each time a number is found in one group which is the same as a number in the group below except for one digit, the numbers pair is ticked and a new composite is created.

This composite number has the same number of digits as the numbers in the pair except the digit different which is replaced by an "x".

The above procedure is repeated on the second column to generate a third column.

The next step is **to identify the essential prime implicants**, which can be done using a prime implicant chart.

Where a prime implicant covers a minterm, the intersection of the corresponding row and column is marked with a cross.

Those columns with only one cross identify the essential prime implicants. -> These prime implicants must be in the final answer.

The single crosses on a column are circled and all the crosses on the same row are also circled, indicating that these crosses are covered by the prime implicants selected.

Once one cross on a column is circled, all the crosses on that column can be circled since the minterm is now covered.

If any non-essential prime implicant has all its crosses circled, the prime implicant is redundant and need not be considered further.

Next, a selection must be made from the remaining nonessential prime implicants, by considering how the non-circled crosses can be covered best.

One generally would take those prime implicants which cover the greatest number of crosses on their row.

If all the crosses in one row also occur on another row which includes further crosses, then the latter is said to dominate the former and can be selected.

The dominated prime implicant can then be deleted.

**Example:**  $F(w,x,y,z) = \Sigma(1,4,6,7,8,9,10,11,15)$

• Grouping & Combining the minterms

(a)			(b)			(c)		
0001	1	✓	1, 9	(8)		8, 9, 10, 11	(1, 2)	
0100	4	✓	4, 6	(2)		8, 9, 10, 11	(1, 2)	
1000	8	✓	8, 9	(1)	✓			
			8, 10	(2)	✓			
0110	6	✓						
1001	9	✓	6, 7	(1)				
1010	10	✓	9, 11	(2)	✓			
			10, 11	(1)	✓			
0111	7	✓						
1011	11	✓	7, 15	(8)				
			11, 15	(4)				
1111	15	✓						



# Prime implicants

Decimal	Binary				Term
	w	x	y	z	
1, 9 (8)	—	0	0	1	$x'y'z$
4, 6 (2)	0	1	—	0	$w'xz'$
6, 7 (1)	0	1	1	—	$w'xy$
7, 15 (8)	—	1	1	1	$xyz$
11, 15 (4)	1	—	1	1	$wyz$
8, 9, 10, 11 (1, 2)	1	0	—	—	$wx'$

# Prime implicant chart

		1	4	6	7	8	9	10	11	15
$\checkmark x'y'z$	1, 9	X					X			
$\checkmark w'xz'$	4, 6		X	X						
$w'xy$	6, 7			X	X					
$xyz$	7, 15				X					X
$wyz$	11, 15					*			X	X
$\checkmark wx'$	8, 9, 10, 11					X	X	X	X	
		$\checkmark$	$\checkmark$	$\checkmark$		$\checkmark$	$\checkmark$	$\checkmark$	$\checkmark$	

$$F = x'y'z + w'xz' + wx' + xyz$$

# 3-7 NAND and NOR Implementation

- NAND gate is a universal gate
  - Can implement any digital system

 


Figure 3.18 Logic Operations with NAND Gates

# NAND Gate

- Two graphic symbols for a NAND gate

 


Figure 3.19 Two Graphic Symbols for NAND Gate

# Two-level Implementation

- Two-level logic
  - NAND-NAND = sum of products
  - Example:  $F = AB + CD$
  - $F = ((AB)' (CD)')' = AB + CD$

# Example 3.10

■ Example 3-10: implement  $F(x, y, z) =$

$$F(x, y, z) = \sum(1, 2, 3, 4, 5, 7) \longrightarrow F(x, y, z) = xy' + x'y + z$$

 


Figure 3.21 Solution to Example 3-10

# Procedure with Two Levels NAND

## ■ The procedure


- Simplified in the form of sum of products;
- A NAND gate for each product term; the inputs to each NAND gate are the literals of the term (the first level);
- A single NAND gate for the second sum term (the second level);
- A term with a single literal requires an inverter in the first level.

# Multilevel NAND Circuits

## ■ Boolean function implementation


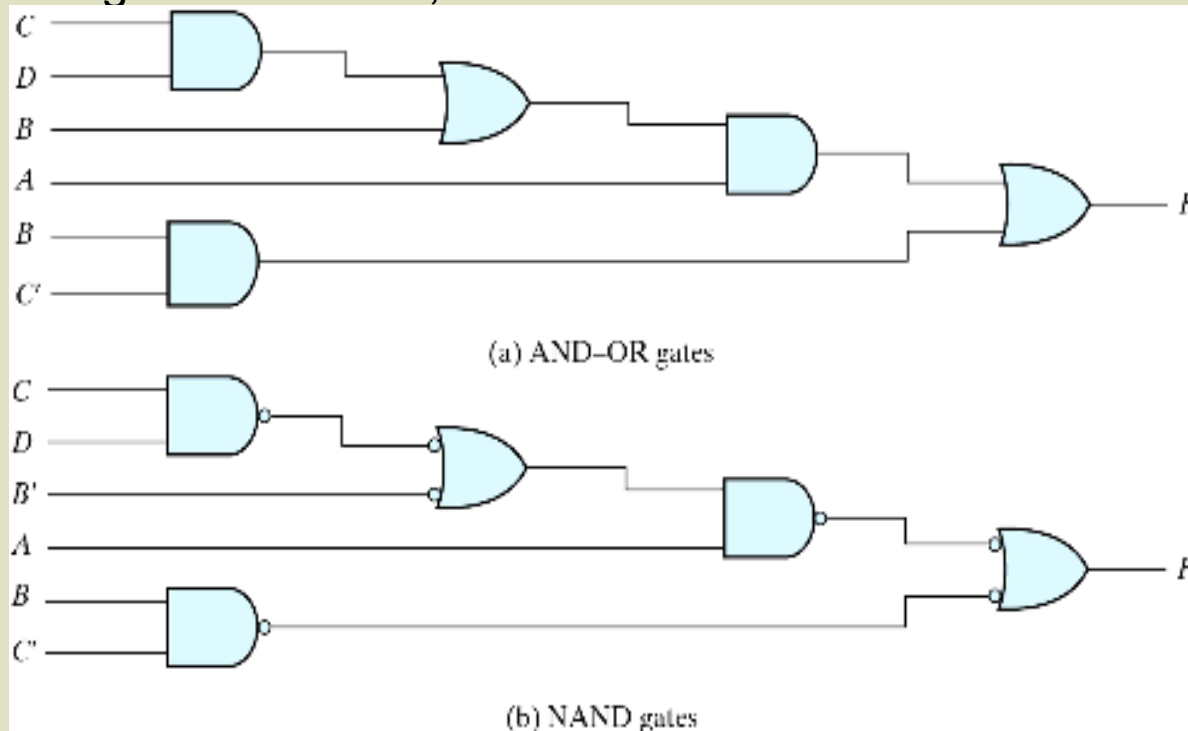
### □ AND-OR logic → NAND-NAND logic

- AND → AND + inverter
- OR: inverter + OR = NAND
- For every bubble that is not compensated by another small circle along the same line, insert an inverter.






# NAND Implementation

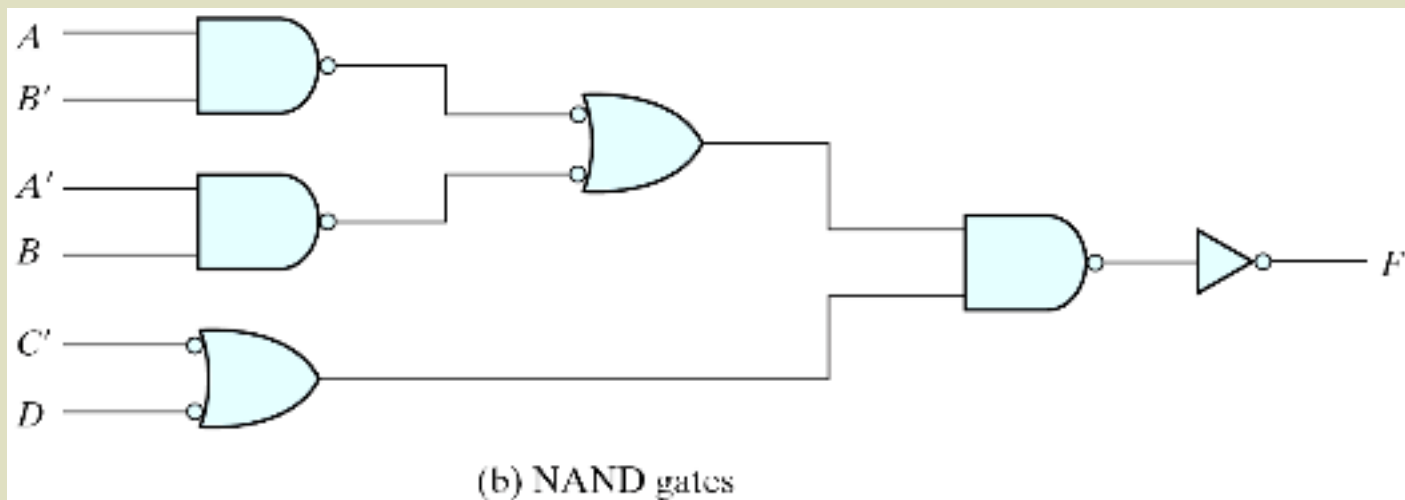 
 
# NOR Implementation

- NOR function is the dual of NAND function.
- The NOR gate is also universal.



# Two Graphic Symbols for a NOR Gate

 


Figure 3.25 Two Graphic Symbols for NOR Gate

Example:  $F = (A + B)(C + D)E$

 


Figure 3.26 Implementing  $F = (A + B)(C + D)E$

# Example

Example:  $F = (AB' + A'B)(C + D')$

 


Figure 3.27 Implementing  $F = (AB' + A'B)(C + D')$  with NOR gates

# 3-8 Other Two-level Implementations (

## ■ Wired logic


- A wire connection between the outputs of two gates
- Open-collector TTL NAND gates: wired-AND logic
- The NOR output of ECL gates: wired-OR logic

$$F = (AB)' \cdot (CD)' = (AB + CD)' = (A' + B')(C' + D')$$

*AND-OR-INVERT function*


$$F = (A + B)' + (C + D)' = [(A + B)(C + D)]'$$

*OR-AND-INVERT function*

 

(a) Wired-AND in open-collector  
TTL NAND gates.

(AND-OR-INVERT)

 

(b) Wired-OR in ECL gates

(OR-AND-INVERT)

Figure 3.28 Wired Logic

# Non-degenerate Forms

- 16 possible combinations of two-level forms
  - Eight of them: degenerate forms = a single operation
    - AND-AND, AND-NAND, OR-OR, OR-NOR, NAND-OR, NAND-NOR, NOR-AND, NOR-NAND.
  - The eight non-degenerate forms
    - AND-OR, OR-AND, NAND-NAND, NOR-NOR, NOR-OR, NAND-AND, OR-NAND, AND-NOR.
    - AND-OR and NAND-NAND = sum of products.
    - OR-NAND      NOR-OR
    - OR-AND and NOR-NOR = product of sums.
    - NAND-AND, AND-NOR

# AND-OR-Invert Implementation

## ■ AND-OR-INVERT (AOI) Implementation

□ NAND-AND = AND-NOR = AOI

□  $F = (AB + CD + E)'$

□  $F' = AB + CD + E$  (sum of products)

 


Figure 3.29 AND-OR-INVERT circuits,  $F = (AB + CD + E)'$

# OR-AND-Invert Implementation

## ■ OR-AND-INVERT (OAI) Implementation

- OR-NAND = NOR-OR = OAI
- $F = ((A+B)(C+D)E)'$
- $F' = (A+B)(C+D)E$  (product of sums)

 


Figure 3.30 OR-AND-INVERT circuits,  $F = ((A+B)(C+D)E)'$



# Tabular Summary and Examples

## ■ Example 3-11: $F = x'y'z' + xyz'$

- $F' = x'y + xy' + z$  ( $F'$ : sum of products)
- $F = (x'y + xy' + z)'$  ( $F$ : AOI implementation)
- $F = x'y'z' + xyz'$  ( $F$ : sum of products)
- $F' = (x + y + z)(x' + y' + z)$  ( $F'$ : product of sums)
- $F = ((x + y + z)(x' + y' + z))'$  ( $F$ : OAI)


# Tabular Summary and Examples

**Table 3.3**


*Implementation with Other Two-Level Forms*

<b>Equivalent Nondegenerate Form</b>		<b>Implements the Function</b>	<b>Simplify <math>F'</math> into</b>	<b>To Get an Output of</b>
<b>(a)</b>	<b>(b)*</b>			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	$F$
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	$F$

 
\*Form (b) requires an inverter for a single literal term.



 (a) Map simplification in sum of products



(b)  $F = (x'y + xy' + z)'$

 

(c)  $F' = [(x + y + z)(x' + y' + z)]'$

# 3-9 Exclusive-OR Function

- Exclusive-OR (XOR)

- $x \oplus y = xy' + x'y$

- Exclusive-NOR (XNOR)

- $(x \oplus y)' = xy + x'y'$

- Some identities

- $x \oplus 0 = x$

- $x \oplus 1 = x'$

- $x \oplus x = 0$

- $x \oplus x' = 1$

- $x \oplus y' = (x \oplus y)'$

- $x' \oplus y = (x \oplus y)'$

- Commutative and associative


- $A \oplus B = B \oplus A$

- $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$

# Exclusive-OR Implementations
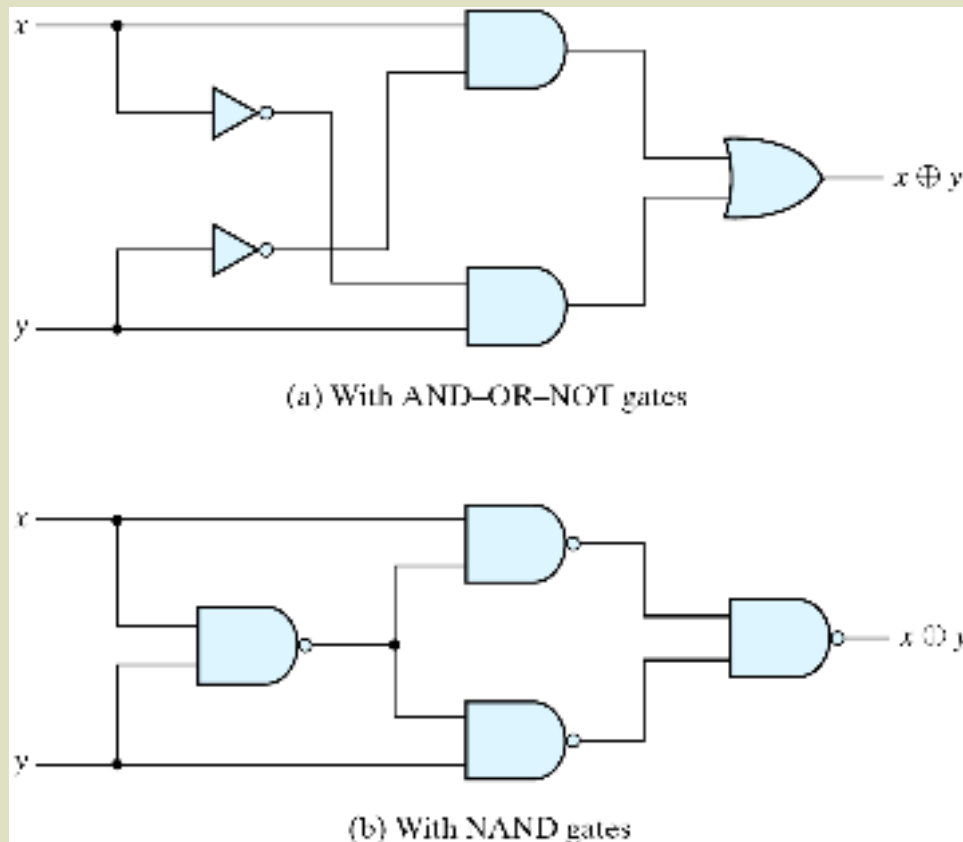
## ■ Implementations

□  $(x' + y')x + (x' + y')y = xy' + x'y = x \oplus y$



# Odd Function

- $A \oplus B \oplus C = (AB' + A'B)C' + (AB + A'B')C = AB'C' + A'BC' + ABC + A'B'C = \Sigma(1, 2, 4, 7)$
- XOR is an odd function  $\rightarrow$  an odd number of 1's, then  $F = 1$ .
- XNOR is an even function  $\rightarrow$  an even number of 1's, then  $F = 1$ .

BC		B			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

(a) Odd function  $F = A \oplus B \oplus C$

BC		B			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

(b) Even function  $F = (A \oplus B \oplus C)'$

Figure 3.33 Map for a Three-variable Exclusive-OR Function

# XOR and XNOR

- Logic diagram of odd and even functions

 


Figure 3.34 Logic Diagram of Odd and Even Functions

# Four-variable Exclusive-OR function

## ■ Four-variable Exclusive-OR function

$$\square A \oplus B \oplus C \oplus D = (AB' + A'B) \oplus (CD' + C'D) = (AB' + A'B)(CD + C'D') + (AB + A'B')(CD' + C'D)$$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$	$m_1$ 1	$m_3$	$m_2$ 1
	01	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$
	11	$m_{12}$	$m_{13}$ 1	$m_{15}$	$m_{14}$ 1
	10	$m_8$ 1	$m_9$	$m_{11}$ 1	$m_{10}$
		D			

(a) Odd function  $F = A \oplus B \oplus C \oplus D$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$ 1	$m_1$	$m_3$ 1	$m_2$
	01	$m_4$	$m_5$ 1	$m_7$	$m_6$ 1
	11	$m_{12}$ 1	$m_{13}$	$m_{15}$ 1	$m_{14}$
	10	$m_8$	$m_9$ 1	$m_{11}$	$m_{10}$ 1
		D			

(b) Even function  $F = (A \oplus B \oplus C \oplus D)'$

Figure 3.35 Map for a Four-variable Exclusive-OR Function



# Parity Generation and Checking

## ■ Parity Generation and Checking

- A parity bit:  $P = x \oplus y \oplus z$
- Parity check:  $C = x \oplus y \oplus z \oplus P$ 
  - $C=1$ : one bit error or an odd number of data bit error
  - $C=0$ : correct or an even # of data bit error

 


Figure 3.36 Logic Diagram of a Parity Generator and Checker

# Parity Generation and Checking

**Table 3.4**

*Even-Parity-Generator Truth Table*

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>p</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

# Parity Generation and Checking

**Table 3.5**

*Even-Parity-Checker Truth Table*

Four Bits Received				Parity Error Check
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0